



# **POWER ENGINEERING**

## **#11 THREE-PHASE TRANSFORMERS**

2018



University  
of Glasgow

# Tesla Quote of the Day

***“Let the future tell the truth, and evaluate each one according to his work and accomplishments. The present is theirs; the future, for which I have really worked, is mine”***





# Transformers

As we saw in lecture 2 the transformer is one of the principal reasons behind the adoption of AC power systems. Its ability to provide a (relatively!) cheap and reliable means of converting AC voltage levels results in high efficiency AC power transmission.

*Over the next 4 lectures we will investigate:*

- Types of Transformers
- The Ideal Transformer
- Basic Electromagnetics
- Transformer Limits
- The Equivalent Circuit for a practical Transformer
- Transformer performance under load: Efficiency & Regulation
- Tests to determine the Equivalent Circuit
- Three Phase Transformers


**Today**

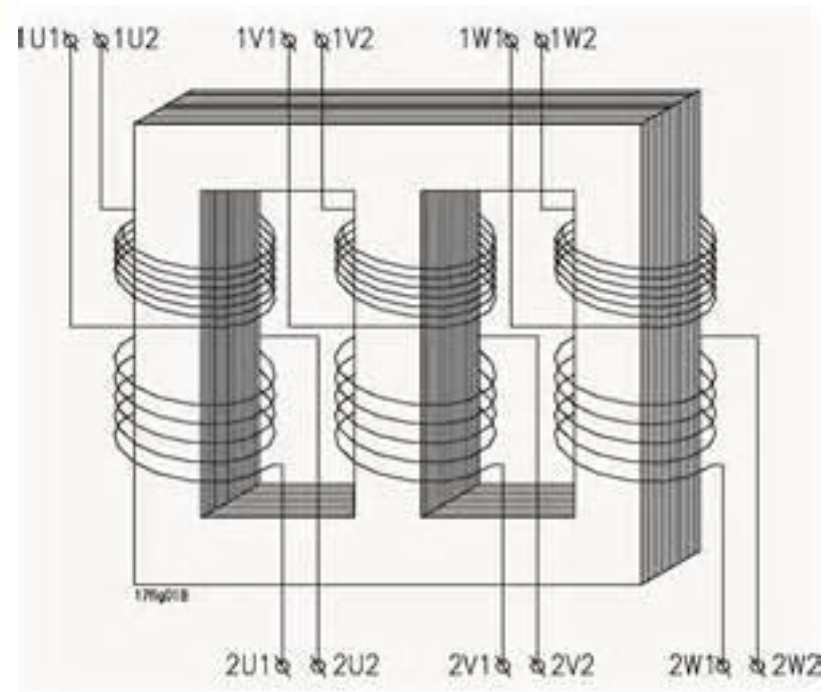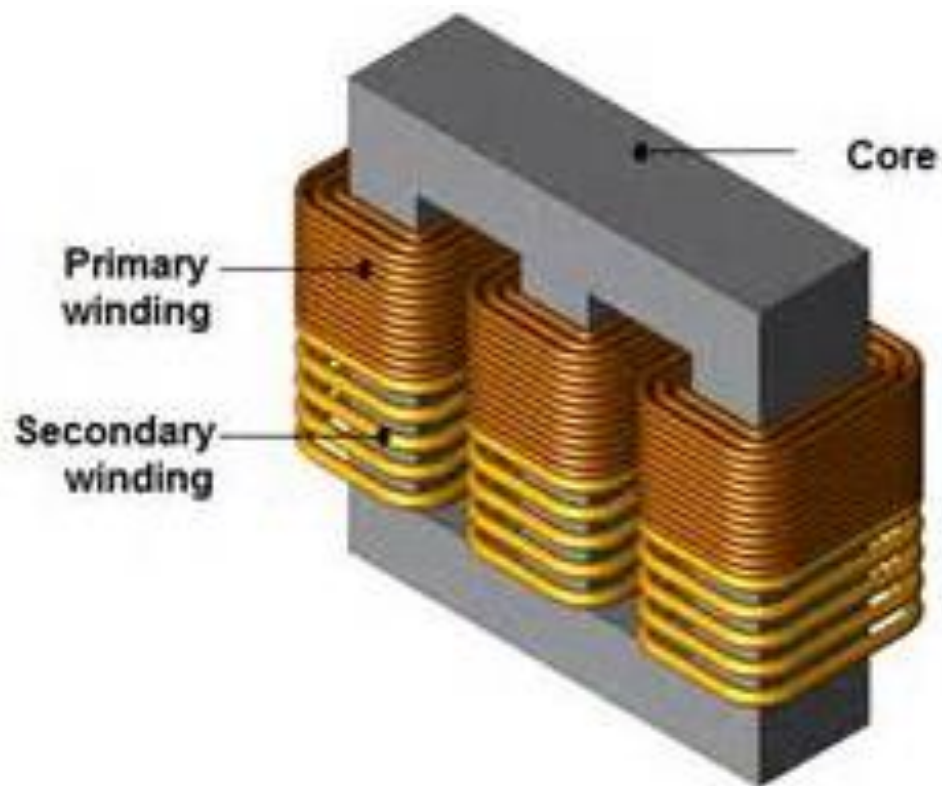

# 3 Phase Transformers

## Option 1

3 x Single Phase Transformers

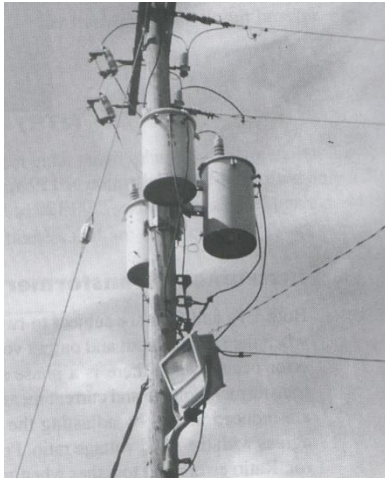


Advantages:

- Only need to replace one transformer when faulty

## Option 2

1 x Three Phase Transformers

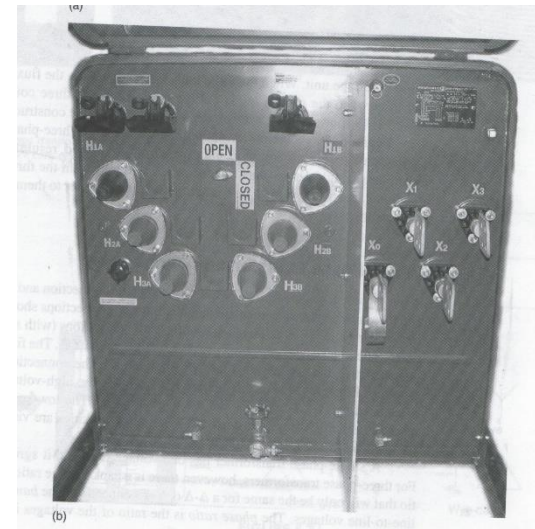


Advantages:

- Smaller and cheaper option (due to common iron core)


## Connection Options:

  $\Delta\Delta$  - Delta/Delta

  $YY$  - Star/Star


  $\Delta Y$  - Delta/Star

  $Y\Delta$  - Star/Delta

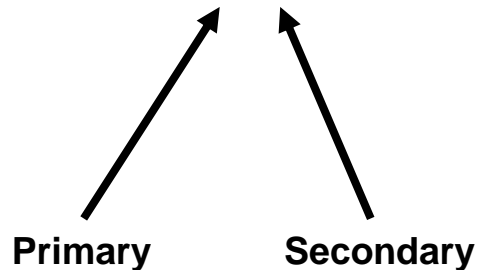

Primary

Secondary

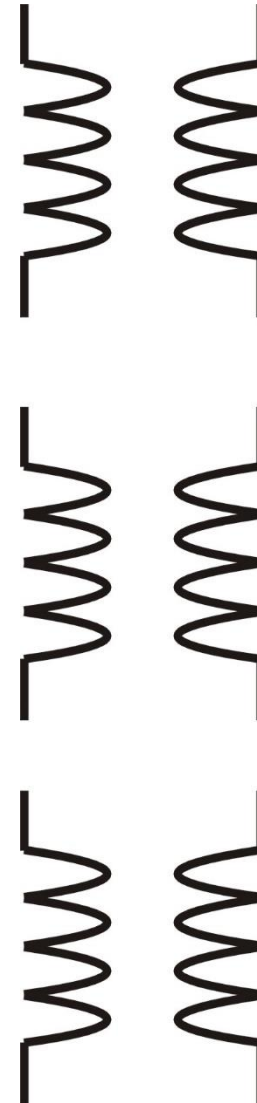

# 3 Phase Transformers: Nameplate Information

**Supply frequency**

**VA Rating**

**Input Line Voltage Rating**

**Input Line Current Rating**

**Output Line Voltage Rating**

**Output Line Current Rating**

**Connection type eg  $\Delta Y$**

**GENERAL ELECTRIC**  
TRANSFORMER

NO. 229A15A CLASS OA THREE-PHASE 60 HERTZ

VOLTAGE RATING 6900 — 480Y / 277 ALL WINDINGS ALUMINUM

KVA RATING 750 CONTINUOUS 65 C RISE SELF COOLED

KVA RATING 862 CONTINUOUS 65 C RISE FUTURE FORCED AIR

HIGH VOLTAGE CONNECTION		
VOLTS	AMP 750 KVA	TAP CHANGER POSITION
7245	59.8	1
7070	61.2	2
6900	62.8	3
6730	64.3	4
6555	66.1	5

LOW VOLTAGE CONNECTION

VOLTS	AMP 750 KVA
480Y / 277	902

LIQUID LEVEL BELOW TOP SURFACE OF HIGHEST POINT OF HANDHOLE FLANGE AT 25°C IS 12.25 INCHES.

LIQUID LEVEL CHANGES .30 INCH PER 10°C CHANGE IN LIQUID TEMPERATURE.

MAXIMUM OPERATING PRESSURES OF LIQUID PRESERVATION SYSTEM 5 POUNDS POSITIVE TO 5 POUNDS NEGATIVE.

TANK SUITABLE FOR 5 POUNDS VACUUM FILLING.

IMPEDANCE VOLTS 6.5 PER CENT AT RATED VOLTS AT 750 KVA

CAUTION! BEFORE INSTALLING OR OPERATING READ INSTRUCTIONS

APPROX. WEIGHTS IN POUNDS

TOTAL	4700
UNTANKING	1950
TANK AND FITTINGS	1600
10C OIL 150 GAL	1150

NP 229A9856

ROME, GEORGIA

MADE IN U. S. A.

Note: VA Rating =  $\sqrt{3} \cdot V_L \cdot I_L$  for 3 phase transformers




# Definitions:

Bank Ratio:

$$\frac{V_{LP}}{V_{LS}}$$

Phase Ratio:
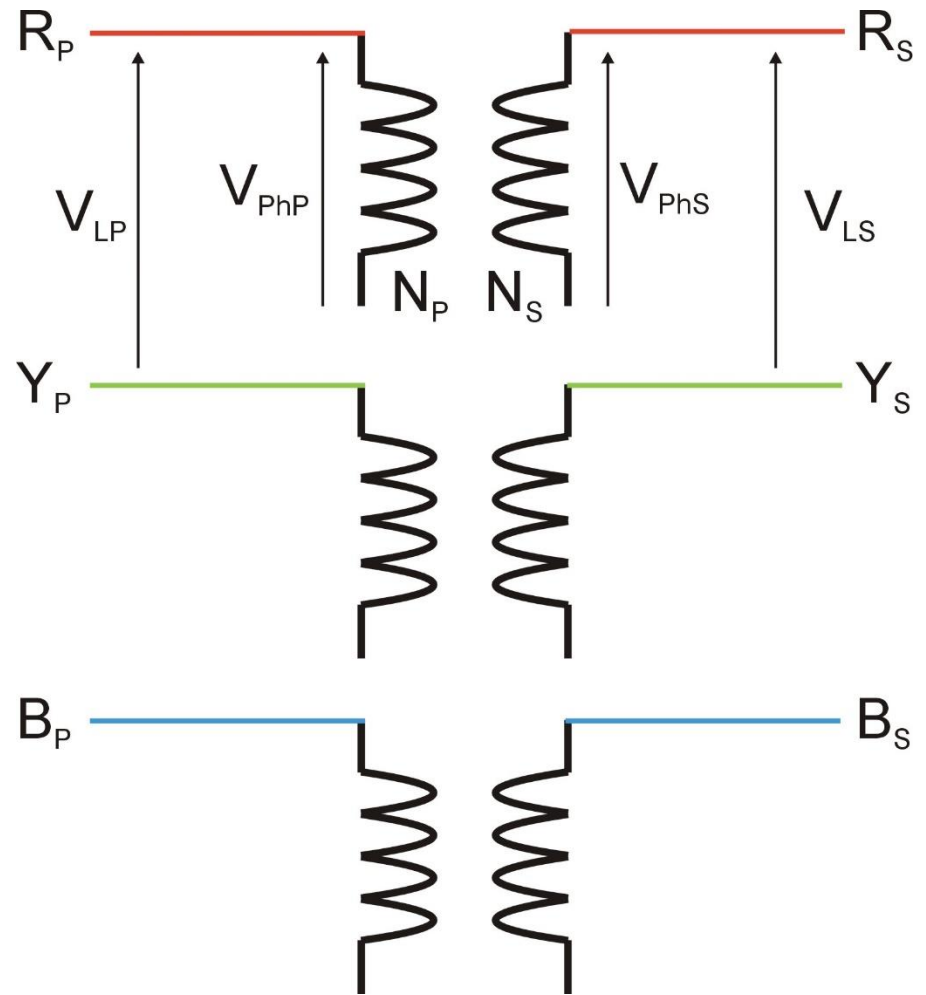
$$\frac{V_{PhP}}{V_{PhS}} = \frac{N_P}{N_S}$$







Note: Bank Ratio is only equal to Phase Ratio for  $\Delta\Delta$  or  $YY$  connections






## $\Delta\Delta$ - Delta/Delta

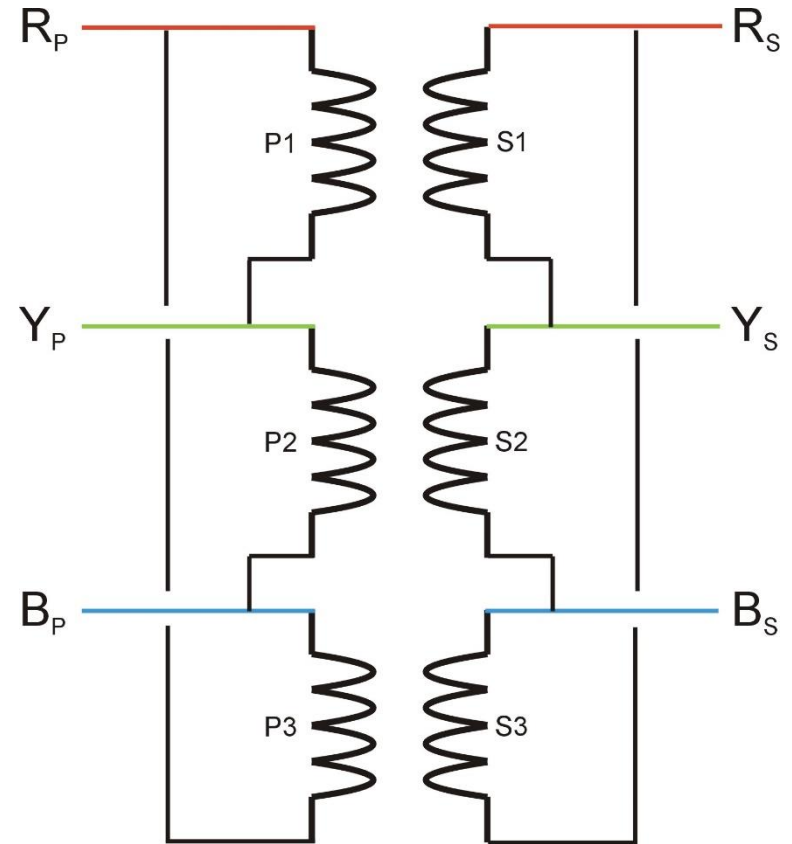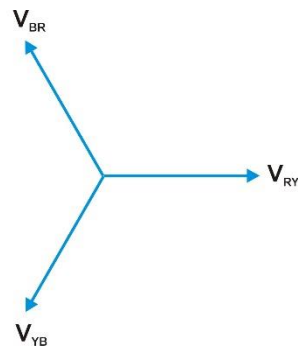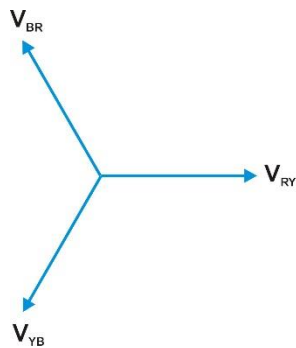
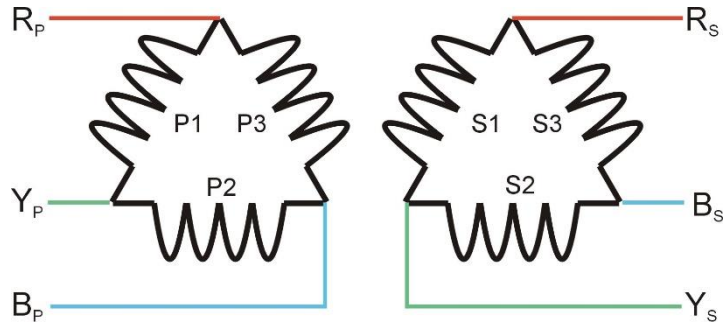


 No Phase Shift between Primary & Secondary Line Voltages

 Bank Ratio = Phase Ratio





## YY - Star/Star

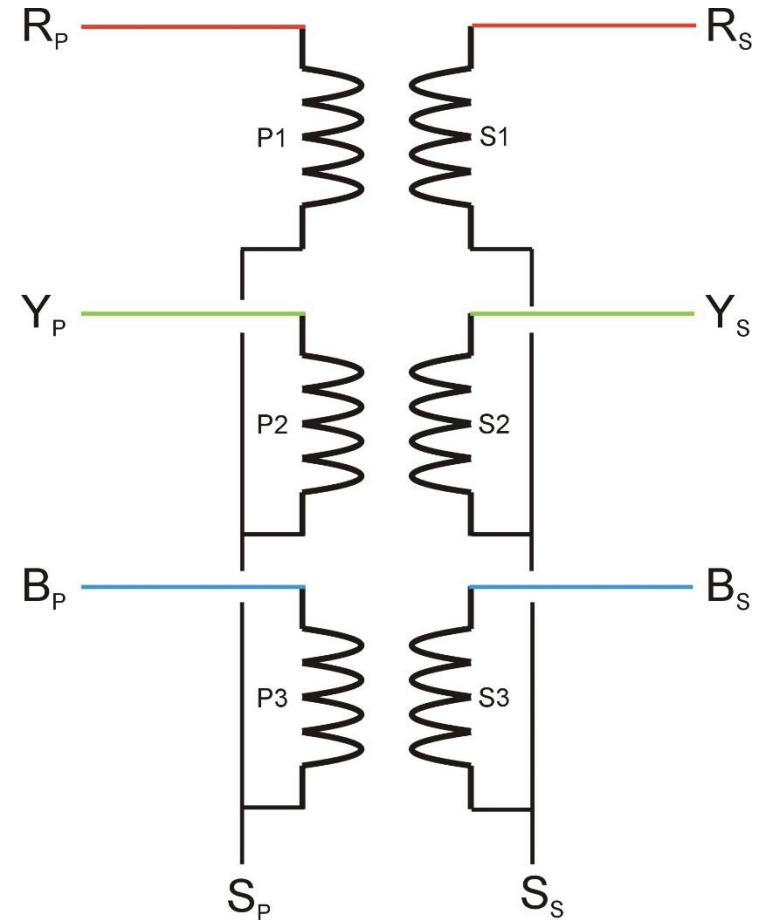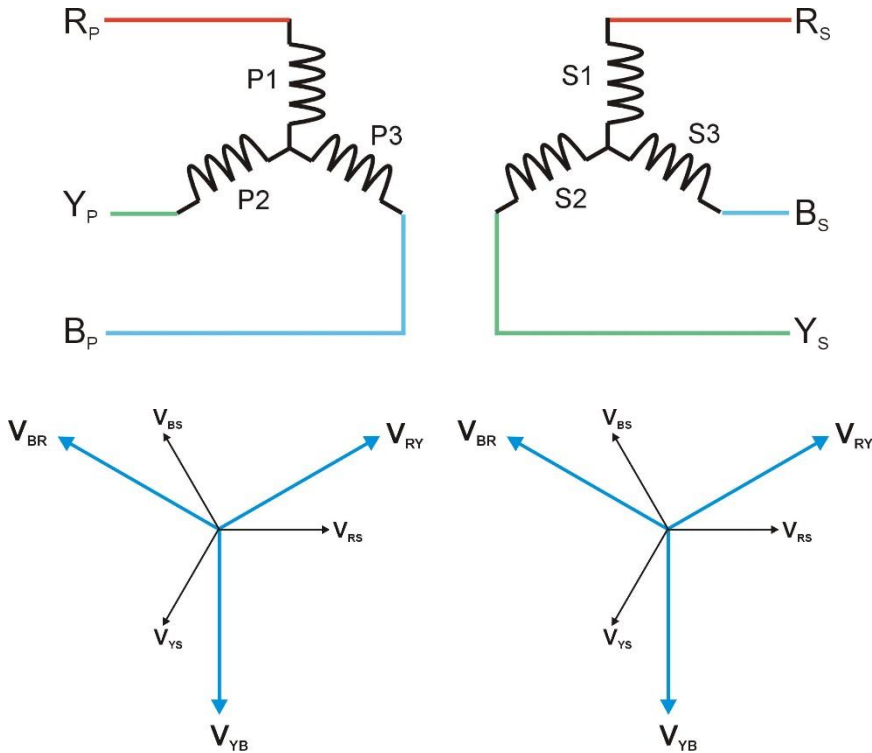

■ No Phase Shift between Primary & Secondary Line Voltages

■ Bank Ratio = Phase Ratio

## $\Delta Y$ - Delta/Star

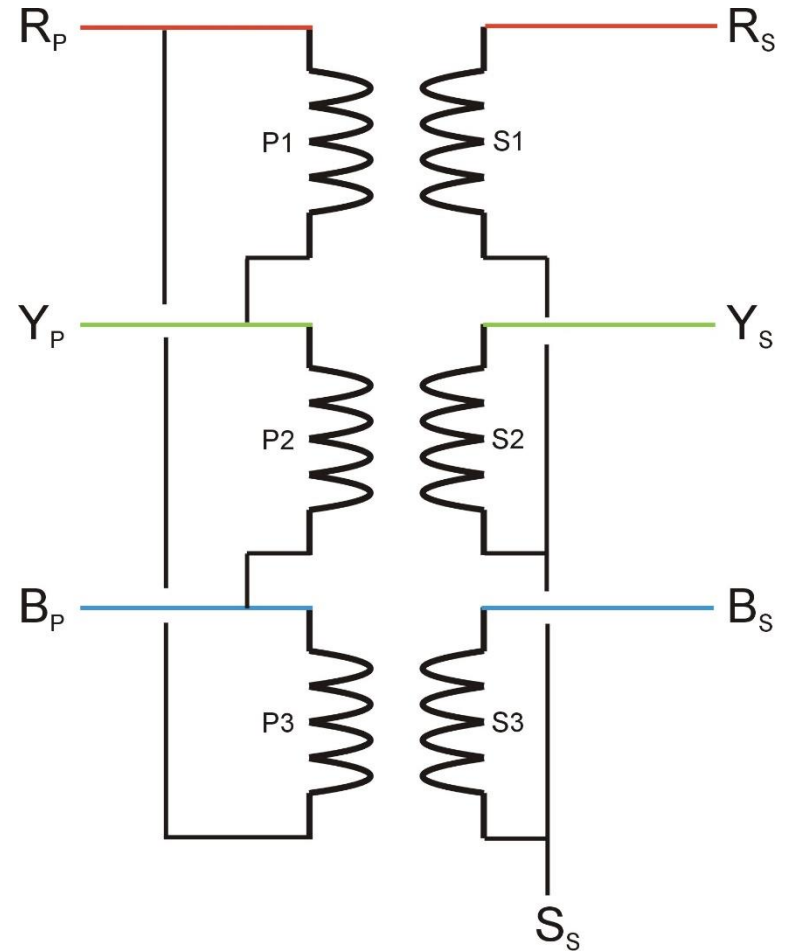
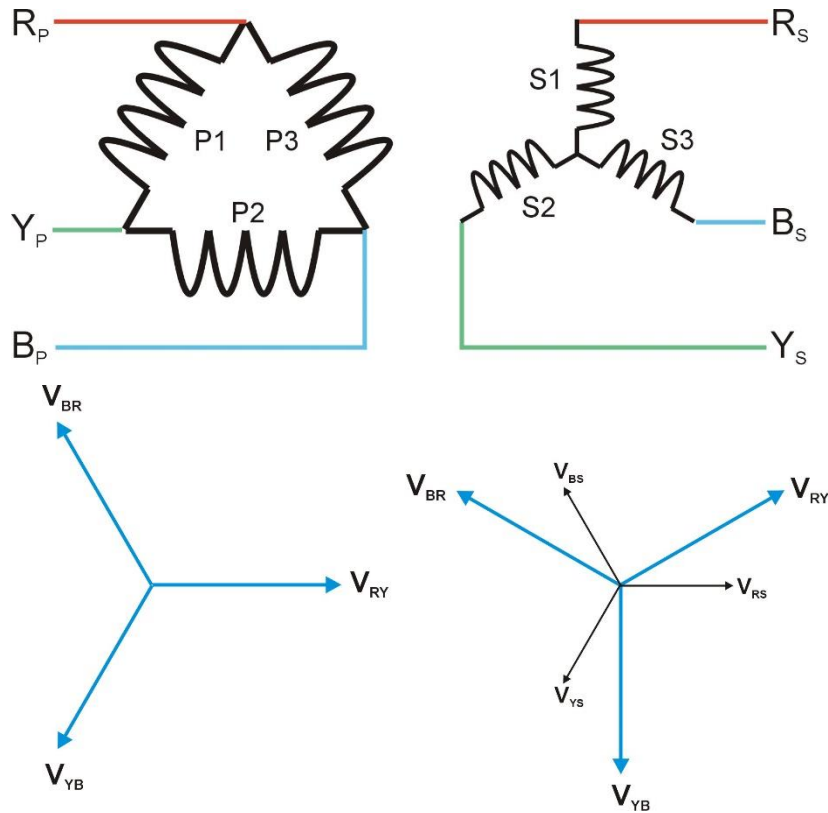


Secondary Line Voltages LEAD Primary Line Voltages by  $30^\circ$

Bank Ratio = Phase Ratio/ $\sqrt{3}$



## $Y\Delta$ - Star/Delta

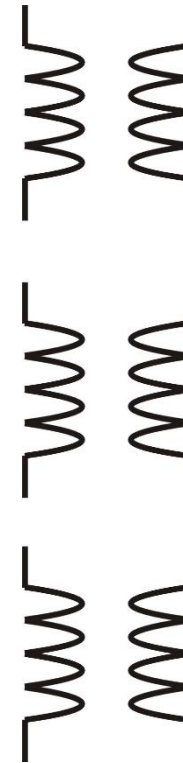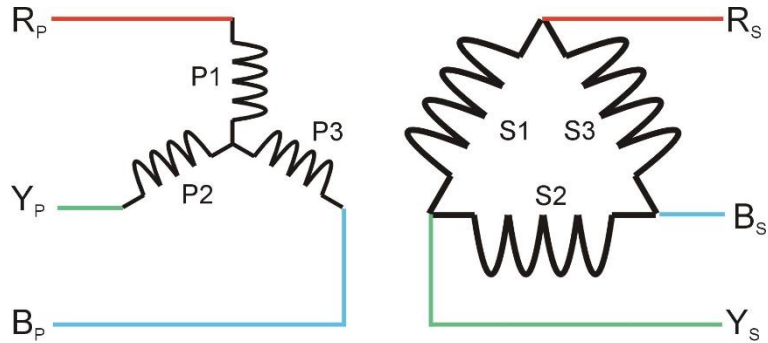

Secondary Line Voltages


Primary Line Voltages by

Bank Ratio =



# Notes on Application of 3 Phase Transformers #1

## Transformer Insulation Voltage Limit

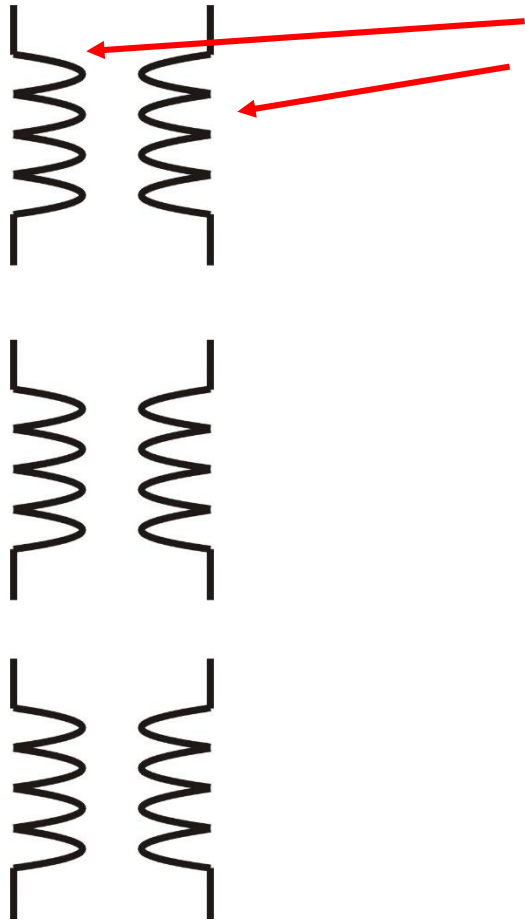

We generally want to keep the voltage across the primary and secondary windings as low as possible to minimise the insulation requirements

This is a bigger issue on the High Voltage (HT) side of the transformer

Therefore it is advantageous to have only the PHASE voltage ( $V_L/\sqrt{3}$ ) across the windings on the HT side:


Step Up Application: Use  $\Delta Y$  connection

Step Down Application: Use  $Y\Delta$  connection

# Notes on Application of 3 Phase Transformers #2
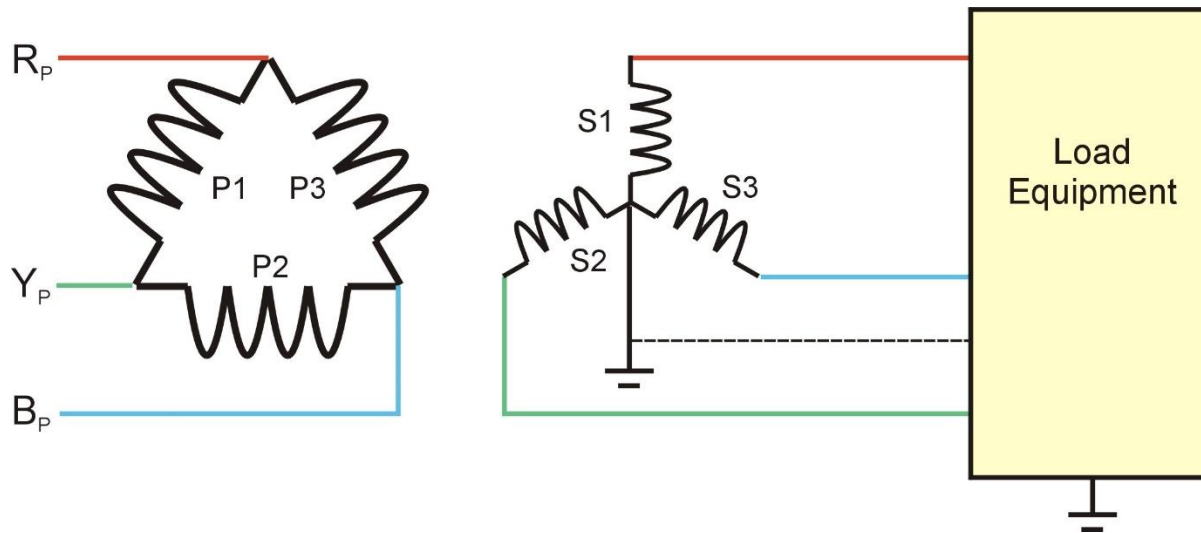
## Grounded Secondary


In some situations (safely) it is desirable to have a grounded neutral point connection on the Secondary windings. This therefore requires either the YY or  $\Delta Y$  connection:



# Notes on Application of 3 Phase Transformers #3
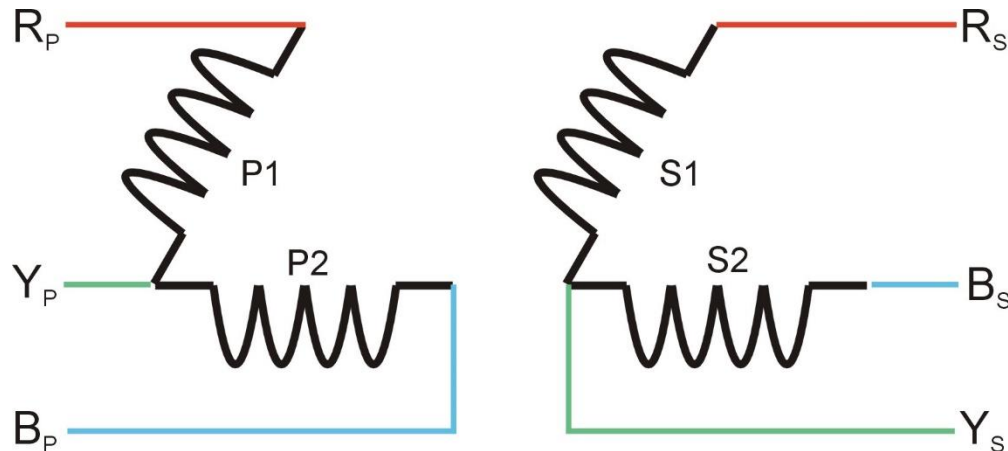
## Open Delta configuration

If 3 single phase transformers are connected as  $\Delta\Delta$  and one of them becomes defective and has to be removed it is possible to feed the 3 phase load on a temporary basis with the two remaining transformers (an advantage of  $\Delta\Delta$ ):




Note that when operating in Open Delta **the three-phase transformers** have to be *de-rated* to **57.7%** of their nominal rating. For example if each transformer is rated at 50kVA then the maximum 3 phase load must not exceed 86.7kVA



# Notes on Application of 3 Phase Transformers #4
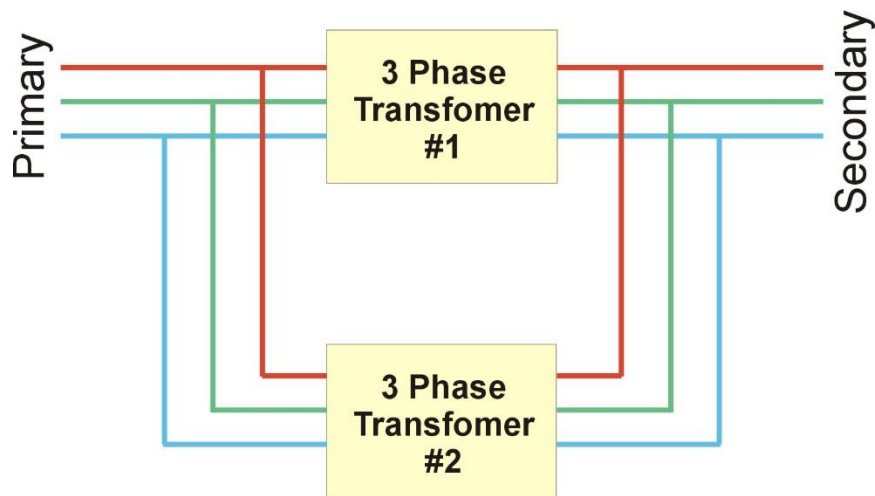
## Parallel connection of transformer secondary windings

Care has to be taken when considering connecting the secondary windings of 3 phase transformers in parallel (sourced from the same 3 phase primary supply) – this being due to the different phase shifts for each of the connection:




	$\Delta\Delta$	YY	$\Delta Y$	$Y\Delta$
$\Delta\Delta$				
YY				
$\Delta Y$				
$Y\Delta$				

**Note: Secondary line voltage magnitudes also need to be equal in ALL cases!**
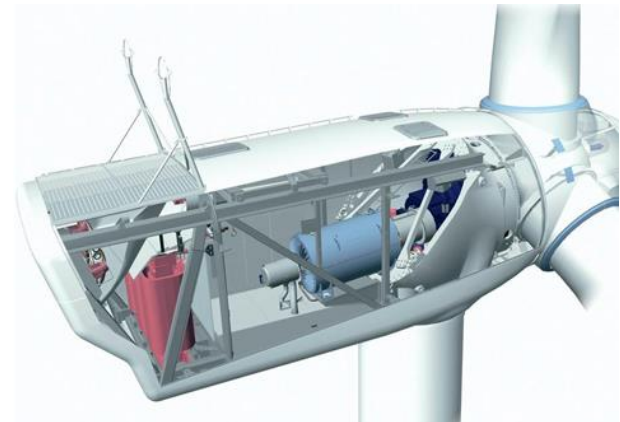
## Example 1

3 phase transformers are required to convert large ( $>1\text{MW}$ ) wind turbine generator voltages to grid voltages. Calculate the bank ratio and phase ratio for a  $690\text{V}/33\text{kV}$   $\Delta Y$  connected transformer.



Solution done on whiteboard during lecture

## Example 2

A three phase  $\Delta Y$  transformer bank is rated 4160V/208V and delivers 300kVA to a balanced delta connected load at rated voltage. Assuming an ideal transformer calculate the following:

1. The magnitudes of the load phase currents
2. The magnitudes of the secondary line current
3. The magnitudes of the primary line current
4. The magnitudes of the currents in the primary coils of the transformer

Solution done on whiteboard during lecture

### Example 3

A three phase  $\Delta\Delta$  transformer consists of three single phase units, each rated at 33.33kVA, 4160V/480V. Determine the rated secondary line current and the rated current in each of the secondary windings.

Solution done on whiteboard during lecture

### Example 4

Due to maintenance requirements one of the transformers in Example 3 is removed and the remaining two transformers are connected in Open Delta. Determine the maximum secondary line current and VA rating for the remaining pair of 33.33kVA transformers?

Solution done on whiteboard during lecture