

# Power Engineering 3

## Tutorial 2: 3 Phase Systems

- Q1 For a 3 phase system with a phase voltage of 10kV determine the line currents, draw the resultant phasor diagram (to scale) and calculate the total (real) power (W) for a balanced star (wye) connected load of  $10 + j20$ .
- Q2 Each phase of a 3 phase delta connected load can be represented by a  $50\Omega$  resistor in series with a 60mH inductor. Determine the following for connection to a 440V/50Hz 3 phase supply:
1. Load Phase Currents  $I_{RY}$ ,  $I_{YB}$  and  $I_{BR}$
  2. The phasor diagram (to scale) and from this determine the line currents  $I_R$ ,  $I_Y$  and  $I_B$
  3. The Apparent Power (VA), Real Power (W) and Reactive Power (VAR) in each phase

( note: if not stated then ALWAYS assume that the given voltage is the LINE voltage  $V_L$  )

- Q3 A star connected load has a wire connecting the star point to the neutral of a 400V/50Hz 3 phase supply. The load on the red phase is 10, the load on the yellow phase is  $7 + j5$  and the load on the blue phase is  $15 - j3$ . Calculate the line currents ( $I_R$ ,  $I_Y$  and  $I_B$ ), sketch the phasor diagram to scale and from this estimate the magnitude of the Star/Neutral current  $I_{SN}$ . Suggest a suitable diameter of wire for the Star/Neutral connection.
- Q4 The load in Q3 is now delta connected. Calculate the load phase currents and construct a scaled phasor diagram to determine the line currents. Calculate the total load power (W) and from the phasor diagram show that the 2 Wattmeter method correctly predicts (allowing for estimation errors!) the total load power for an unbalanced delta connected load.
- Q5 A large single phase load (represented by a resistance of  $0.3\Omega$ ) is to be connected to a three phase 415V/50Hz system. Determine the necessary (delta connected) Capacitance and Inductance reactances to give balanced conditions. Calculate the resultant load phase currents and from a scaled phasor diagram plot and estimate the three line currents.
- Q6 Construct the phasor diagram for a balanced star connected load with lagging currents and prove that the 2 Wattmeter method correctly calculates the total power loss in the 3 phase load. (Note: I did a similar proof for a balanced Delta connected load in Lecture 5).