

## Power Eng 3


### Tutorial 2 solutions

①

#### Power Eng 3


#### TUTORIAL 2: 3 PHASE SYSTEMS

Q1

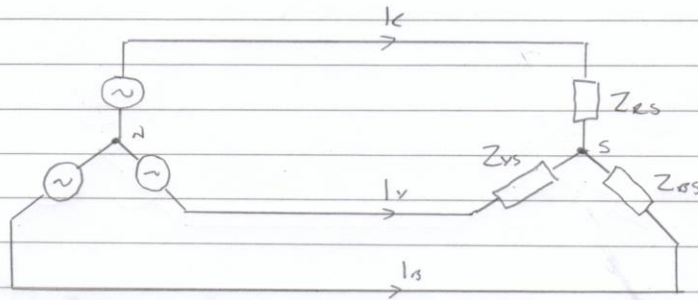

$$Z_{Ls} = Z_{Ys} = Z_{Bs} = 10 + j20$$
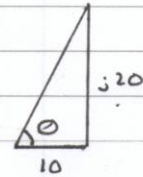
$$\Rightarrow Z_{Ls} \text{ etc} = 22.4 \angle 63.4^\circ$$



$$V_{LN} = 10,000 \angle 0^\circ$$

$$\Rightarrow \bar{I}_L = \frac{\bar{V}_{LN}}{Z_{Ls}} = \frac{10,000 \angle 0^\circ}{22.4 \angle 63.4^\circ} = 446 \angle -63.4^\circ$$

$$\Rightarrow \bar{I}_Y = 446 \angle (-63.4 - 120) = 446 \angle -183^\circ$$

$$\Rightarrow \bar{I}_B = 446 \angle (-63.4 + 120) = 446 \angle 56.6^\circ$$


$$P_T = 3 |V_{LN}| |I_L| \cos \phi$$

$$\Rightarrow P_T = 3 \times 10,000 \times 446 \times \cos(-63.4)$$

$$\Rightarrow P_T = \underline{\underline{5.99 \text{ MW}}}$$

②


Q1 Phasor Diagram:

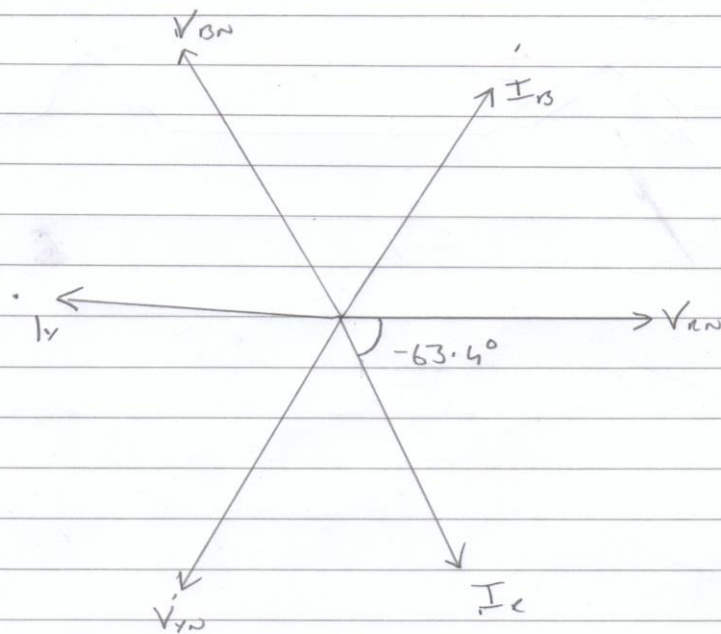

Scale:  $1\text{cm} \equiv 2000\text{V}$   
 $1\text{cm} \equiv 100\text{A}$

3


Q2

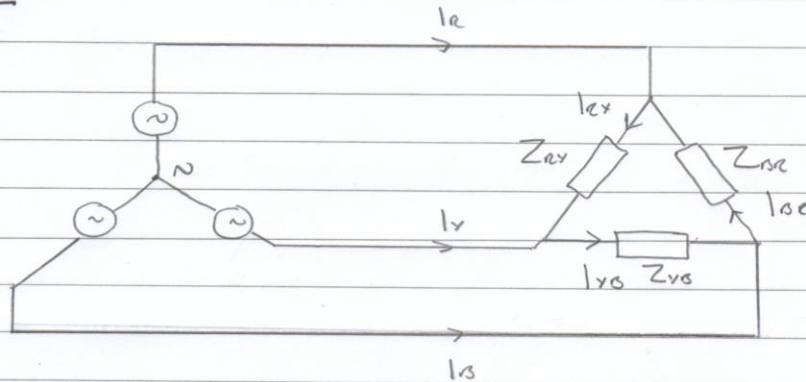

$$Z_{ey} = Z_{yn} = Z_{en} = R + jX_L$$

$$X_L = \omega L = 2\pi \times 50 \times 60 \times 10^{-3} = 18.8 \Omega$$
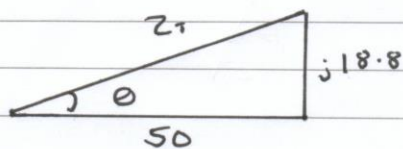
$$\Rightarrow Z_{ey} \text{ etc} = 50 + j18.8 = 53.4 \angle 20.6^\circ$$



$$\Rightarrow \bar{I}_{ey} = \frac{\bar{V}_{ey}}{Z_{ey}} = \frac{440 \angle 30^\circ}{53.4 \angle 20.6^\circ} = 8.24 \angle 9.4^\circ$$

$$\Rightarrow \bar{I}_{yn} = 8.24 \angle (9.4 - 120) = 8.24 \angle -110.6^\circ$$

$$\Rightarrow \bar{I}_{ne} = 8.24 \angle (9.4 + 120) = 8.24 \angle 129.4^\circ$$

Line currents ( $I_L$  etc) are  $\sqrt{3} \times$  Load Phase currents ( $I_{ph}$  etc) and lag by  $30^\circ$


④

$$\bar{I}_R = \sqrt{3} \times 8.24 \angle (9.4 - 30) = 14.2 \angle -20.6^\circ$$

$$\bar{I}_Y = 14.2 \angle (-20.6 - 120) = 14.2 \angle -140.6^\circ$$

$$\bar{I}_B = 14.2 \angle (-20.6 + 120) = 14.2 \angle 99.4^\circ$$

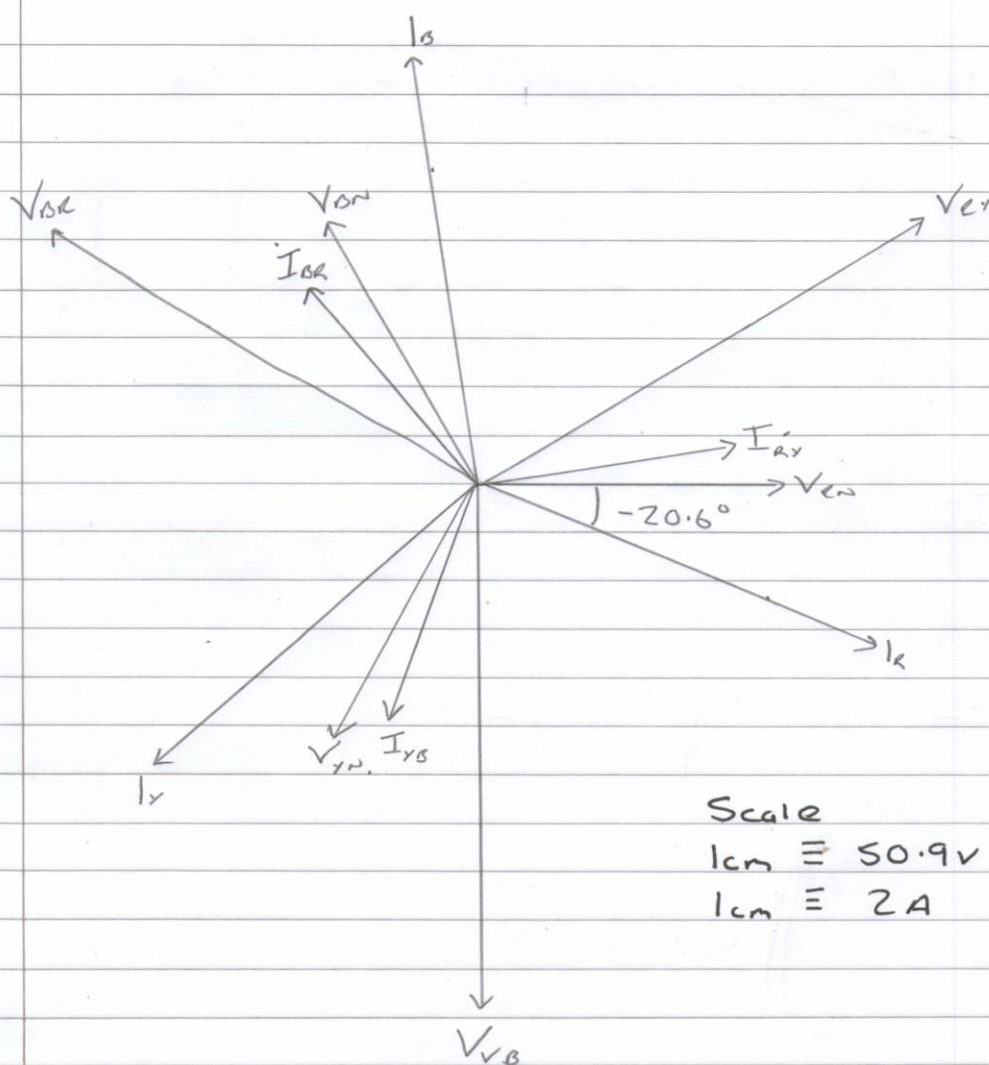(Note alternatively  $I_R$  etc could be determined from scaled phasor diagram but for BALANCED case I would suggest doing as above)



(Hint: Always make  $V_{R'}$  etc  $5\text{cm}$  +  $V_{R'}$  etc  $8.6\text{cm}$ )



⑤

$$\text{APPARENT POWER} = |V_{\text{en}}| |I_c|$$

(S)

$$= \frac{440}{\sqrt{3}} \times 14.2$$

$$= 254 \times 14.2$$

$$= \underline{\underline{3.6 \text{ kVA}}}$$

$$\text{REAL POWER} = S \cdot \cos \phi \leftarrow \begin{array}{l} \text{Angle} \\ \text{between} \\ V_{\text{en}} \text{ \& } I_c \end{array}$$

(P)

$$= 3600 \times \cos(-20.6)$$

$$= \underline{\underline{3.37 \text{ kW}}}$$

$$\text{REACTIVE POWER} = -S \cdot \sin \phi$$

(Q)

$$= -3600 \times \sin(-20.6)$$

$$= \underline{\underline{1.27 \text{ kVAR}}}$$


(note these are per phase values)



(6)

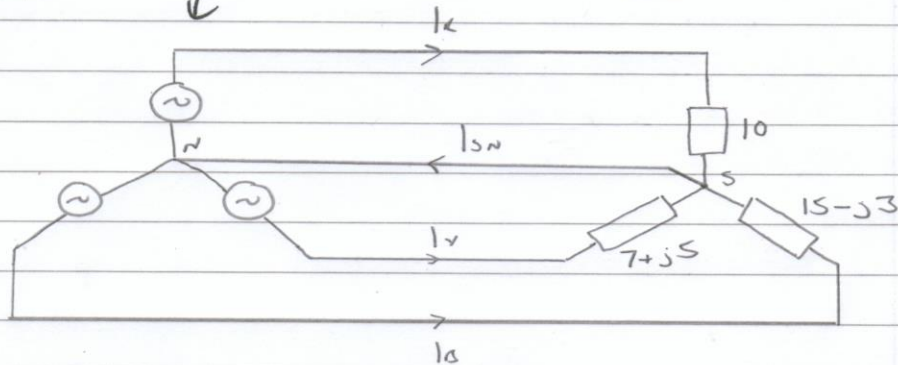
Q3

$$\text{Phase Voltage} = \frac{400}{\sqrt{3}} = 231 \text{ V}$$




$$Z_{rs} = 10 \equiv 10 \angle 0^\circ$$
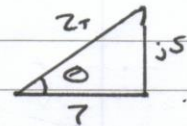
$$Z_{rs} = 7 + j5 \equiv 8.6 \angle 35.5^\circ$$


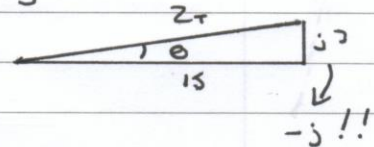
$$Z_{bs} = 15 - j3 \equiv 15.3 \angle -11.3^\circ$$



$$\bar{I}_r = \frac{\bar{V}_{ph}}{Z_{rs}} = \frac{231 \angle 0^\circ}{10 \angle 0^\circ} = 23.1 \angle 0^\circ$$

$$\bar{I}_r = \frac{\bar{V}_{ph}}{Z_{rs}} = \frac{231 \angle -120^\circ}{8.6 \angle 35.5^\circ} = 26.8 \angle -155^\circ$$


$$\bar{I}_s = \frac{\bar{V}_{ph}}{Z_{bs}} = \frac{231 \angle 120^\circ}{15.3 \angle -11.3^\circ} = 15 \angle 131^\circ$$

Now draw Scaled Phasor-Diagram

7

Scale

1cm  $\equiv$  5A

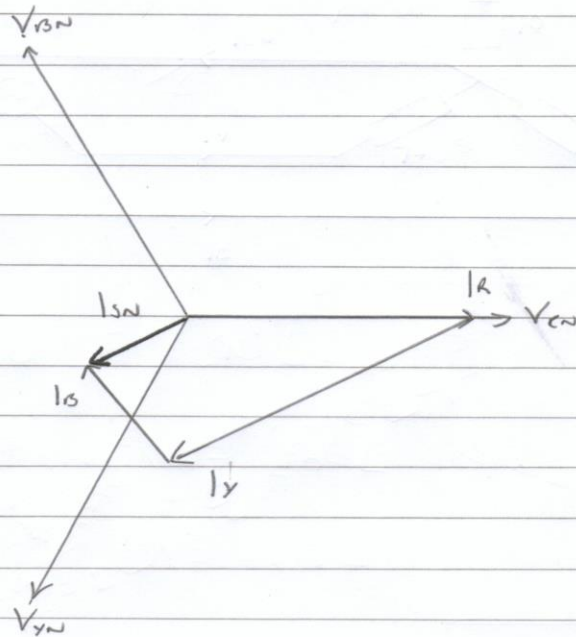

measured  $I_N = 1.8\text{cm} \equiv 9\text{A}$

Based on  $5\text{A/mm}^2$  Current Density

$$\frac{9}{5} = 1.8\text{ mm}^2 \text{ Cross Sectional Area of Wire}$$


$$A = \pi r^2$$

$$\Rightarrow r = \sqrt{\left(\frac{A}{\pi}\right)} = \sqrt{\left(\frac{1.8}{\pi}\right)} = 0.76\text{ mm}$$

$$\Rightarrow \text{Wire Diameter} \approx \underline{\underline{1.5\text{ mm}}}$$



Q4

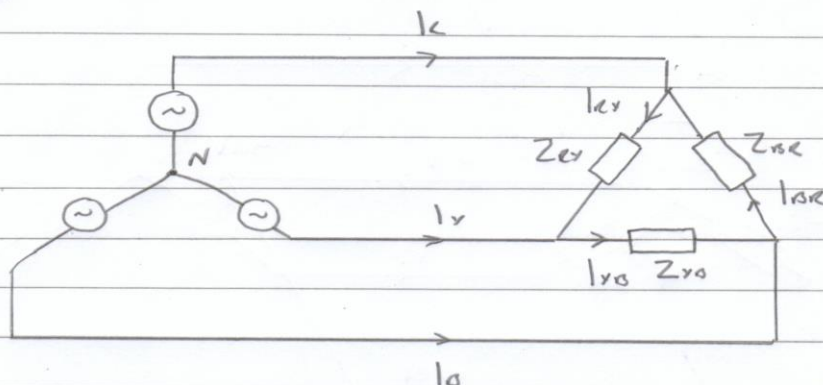

$$V_{\text{rms}} = 400 \text{ V}$$

$$Z_{L1} = 10 \angle 0^\circ = 10 + j0$$

$$Z_{L2} = 8.6 \angle 55.5^\circ = 7 + j5$$

$$Z_{L3} = 15.3 \angle -11.3^\circ = 15 - j3$$

$$\bar{I}_{L1} = \frac{\bar{V}_{L1}}{Z_{L1}} = \frac{400 \angle 30^\circ}{10 \angle 0^\circ} = 40 \angle 30^\circ$$

$$\bar{I}_{L2} = \frac{\bar{V}_{L2}}{Z_{L2}} = \frac{400 \angle -90^\circ}{8.6 \angle 55.5^\circ} = 46.5 \angle -125^\circ$$

$$\bar{I}_{L3} = \frac{\bar{V}_{L3}}{Z_{L3}} = \frac{400 \angle 150^\circ}{15.3 \angle -11.3^\circ} = 26.1 \angle 161^\circ$$

Knowing the load phase currents we can determine the total load power (W)

$$P_T = |I_{L1}|^2 \cdot R_{L1} + |I_{L2}|^2 \cdot R_{L2} + |I_{L3}|^2 \cdot R_{L3}$$


9

$$\Rightarrow P_T = 40^2 \times 10 + 46.5^2 \times 7 + 26.1^2 \times 15$$

$$\Rightarrow P_T = 16,000 + 15,100 + 10,200$$

$$\Rightarrow P_T = \underline{\underline{41.3 \text{ kW}}}$$

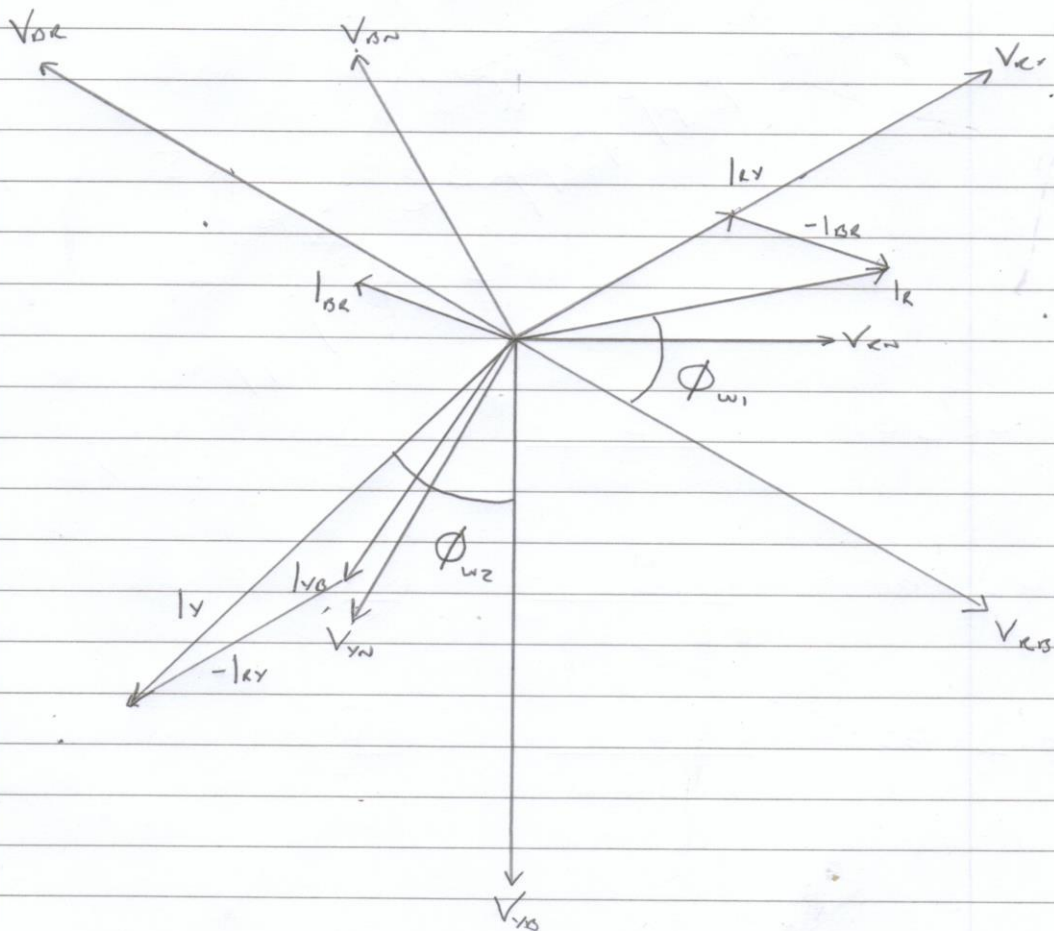Now draw Phasor Diagram to determine line currents



$$\bar{I}_e = \bar{I}_{er} - \bar{I}_{oc}$$

$$\bar{I}_r = \bar{I}_{rs} - \bar{I}_{er}$$

## 2 WATTMETER METHOD:

$$W_1 = |V_{x0}| \cdot |I_x| \cdot \cos \phi_{W_1}$$

angle between  $V_{x0}$  &  $I_x$

$$W_2 = |V_{x0}| \cdot |I_y| \cdot \cos \phi_{W_2}$$

angle between  $V_{x0}$  &  $I_y$

measured from Phasor-Diagram:

$$|I_x| = 6 \text{ cm} \equiv 60 \text{ A}$$

$$|I_y| = 8.4 \text{ cm} \equiv 84 \text{ A}$$

$$\phi_{W_1} = 40^\circ$$

$$\phi_{W_2} = 46^\circ$$

$$\Rightarrow W_1 = 400 \times 60 \times \cos 40^\circ$$

$$\Rightarrow W_1 = 18.4 \text{ kW}$$

$$\Rightarrow W_2 = 400 \times 84 \times \cos 46^\circ$$

$$\Rightarrow W_2 = 23.3 \text{ kW}$$

$$\Rightarrow P_T = W_1 + W_2$$


$$\Rightarrow P_T = 18.4 \text{ kW} + 23.3 \text{ kW}$$

$$\Rightarrow P_T = \underline{\underline{41.7 \text{ kW}}}$$



Allowing for  
estimation  
errors

Q5

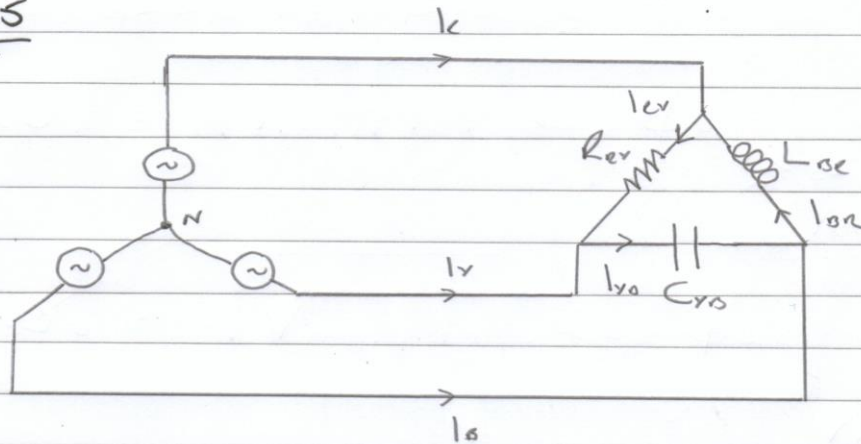

$$X_C = \sqrt{3} \cdot R = \sqrt{3} \times 0.3 = 0.52 \Omega$$

$$X_L = \sqrt{3} \cdot R = \sqrt{3} \times 0.3 = 0.52 \Omega$$

$$\bar{I}_{Yr} = \frac{\bar{V}_{Yr}}{R_{Yr}} = \frac{415 \angle 30^\circ}{0.3 \angle 0^\circ} = 1380 \angle 30^\circ$$


$$\bar{I}_{Yb} = \frac{\bar{V}_{Yb}}{C_{Yb}} = \frac{415 \angle -90^\circ}{0.52 \angle -90^\circ} = 798 \angle 0^\circ$$

$$\bar{I}_{Yr} = \frac{\bar{V}_{Yr}}{L_{Yr}} = \frac{415 \angle 150^\circ}{0.52 \angle 90^\circ} = 798 \angle 60^\circ$$

Now draw Scaled phasor diagram  
to determine line currents  $I_L, I_Y, I_B$



12

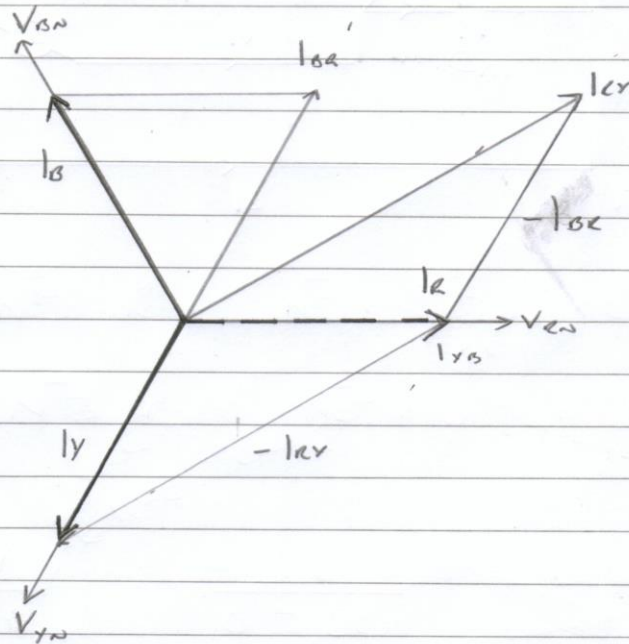


---

---




Q6

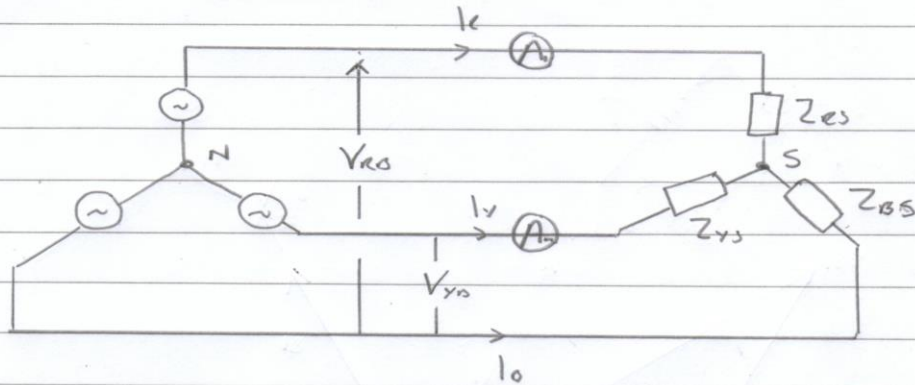

2 WATTMETER METHOD

$$W_1 \rightarrow V_{RS} \times I_R \times \cos \phi_{W1}$$
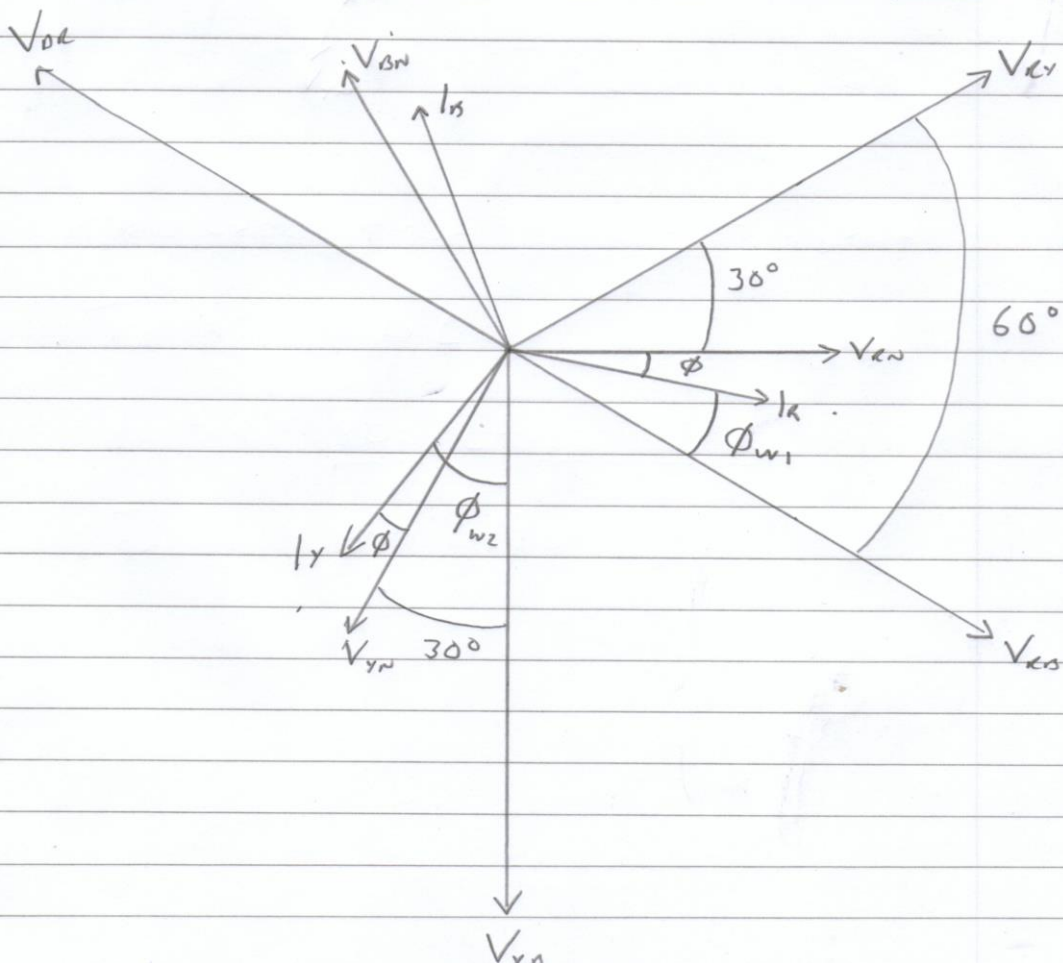
$$W_2 \rightarrow V_{YO} \times I_Y \times \cos \phi_{W2}$$



Prove that Total Real Power

$$P_T = 3 \cdot \underset{V_{ph}}{|V_{ex}|} \cdot \underset{I_L}{|I_L|} \cdot \cos \phi$$

Angle between  $V_{ex}$  &  $I_L$

from Phase-Diagram:

$$\phi_{w_1} + \phi + 30^\circ = 60^\circ$$

$$\Rightarrow \phi_{w_1} = 30^\circ - \phi \quad \text{--- (1)}$$

$$\phi_{w_2} = 30^\circ + \phi \quad \text{--- (2)}$$

$$W_1 = |V_{ex}| \cdot |I_L| \cdot \cos \phi_{w_1}$$

$$\Rightarrow W_1 = |V_L| \cdot |I_L| \cdot \cos (30^\circ - \phi)$$

$$W_2 = |V_{ex}| \cdot |I_L| \cdot \cos \phi_{w_2}$$

$$\Rightarrow W_2 = |V_L| \cdot |I_L| \cdot \cos (30^\circ + \phi)$$

$$P_T = W_1 + W_2$$

$$\Rightarrow P_T = |V_L| \cdot |I_L| \cdot \cos (30^\circ - \phi) + |V_L| \cdot |I_L| \cdot \cos (30^\circ + \phi)$$

Subst-

$$\cos (A - B) = \cos A \cos B + \sin A \sin B$$

$$\cos (A + B) = \cos A \cos B - \sin A \sin B$$

(15)

$$\Rightarrow P_T = |V_L| \cdot |I_L| \cdot (\cos 30^\circ \cos \phi + \cos 30^\circ \cos \phi)$$

$$\Rightarrow P_T = |V_L| \cdot |I_L| \cdot (0.866 \cos \phi + 0.866 \cos \phi)$$

$$\Rightarrow P_T = \sqrt{3} \cdot |V_L| \cdot |I_L| \cos \phi$$

$$\text{Subst } V_L = \sqrt{3} \cdot V_{ph}$$

$$\Rightarrow P_T = \underline{\underline{3 |V_{ph}| \cdot |I_L| \cdot \cos \phi}}$$