

Power Engineering 3

Induction Motor Tutorial Solutions



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.




Subject: INDUCTION MOTOR TUTORIAL

Date: THU 10th MAR

Q1

NO LOAD TEST

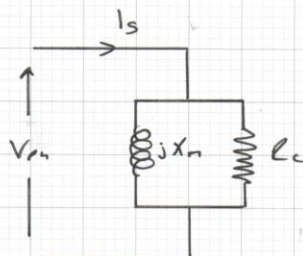

$$P_{in} = \frac{V_{ph}^2}{R_c}$$

$$\Rightarrow R_c = \frac{V_{ph}^2}{P_{in}} = \frac{400^2}{100} = \underline{\underline{1600 \Omega}}$$

$$Q_{in}^2 = S_{in}^2 - P_{in}^2 = (V_{ph} I_s)^2 - P_{in}^2$$

$$\Rightarrow Q_{in}^2 = (400 \times 1)^2 - 100^2 = 150000$$

$$\Rightarrow Q_{in} = 387 \text{ VAR}$$

$$Q_{in} = \frac{V_{ph}^2}{X_m}$$

$$\Rightarrow X_m = \frac{V_{ph}^2}{Q_{in}} = \frac{400^2}{387} = \underline{\underline{413 \Omega}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.




Subject:

Date:

127500

LOCKED ROTOR TEST:

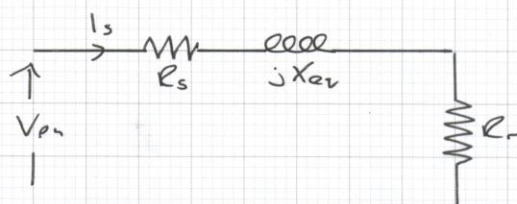

$$P_{in} = I_s^2 (R_s + R_r)$$

$$\Rightarrow (R_s + R_r) = \frac{P_{in}}{I_s^2} = \frac{350}{5^2} = 14 \Omega$$

$$R_s = 6 \Omega \Rightarrow \underline{\underline{R_r = 8 \Omega}}$$

$$Q_{in}^2 = S_{in}^2 - P_{in}^2 = (V_{ph} I_s)^2 - P_{in}^2$$

$$\Rightarrow Q_{in}^2 = (100 \times 5)^2 - 350^2 = 127500$$

$$\Rightarrow Q_{in} = 357 \text{ VAR}$$

$$Q_{in} = I_s^2 X_{eq}$$

$$\Rightarrow X_{eq} = \frac{Q_{in}}{I_s^2} = \frac{357}{5^2} = \underline{\underline{14.3 \Omega}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157 Fax: +44(0)141 330 3158 Email: saffron@elec.gla.ac.uk Web: www.speedlab.co.uk



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject: Date:

$$\begin{aligned}
 \text{vi)} \quad \text{EFFICIENCY} &= \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \times 100\% \\
 &= \frac{30671}{33000} \times 100\% \\
 &= \underline{\underline{92.9\%}}
 \end{aligned}$$

$$\text{Q3 i)} \quad N_s = \frac{120 \times 8s}{p} = \frac{120 \times 50}{4}$$

$$\Rightarrow N_s = 1500 \text{ rpm}$$

$$\text{Slip (s)} = \frac{N_s - N_r}{N_s} = \frac{1500 - 1350}{1500}$$

$$\Rightarrow \text{Slip (s)} = \underline{\underline{0.1}}$$

ii) Need to draw the Equivalent Circuit
and determine I_r



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject: NOTE: 400V IS LINE VOLTAGE

Date:

$$V_{ph} = \frac{400}{\sqrt{3}} = 231V$$

$$Z_T = R_s + jX_{eq} = \frac{R_r}{s} = 5 + j4 + 60$$

$$\Rightarrow Z_T = 65 + j4 = 65.1 \angle 3.5^\circ$$

$$\Rightarrow I_r = \frac{V_{ph}}{Z_T} = \frac{231 \angle 0^\circ}{65.1 \angle 3.5^\circ} = \underline{\underline{3.55 \angle -3.5^\circ}}$$

AIR GAP POWER
$$P_{ag} = \frac{3 I_r^2 R_r}{s}$$

$$= \frac{3 \times 3.55^2 \times 6}{0.1}$$

$$= \underline{\underline{2268W}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157 Fax: +44(0)141 330 3158 Email: saffron@elec.gla.ac.uk Web: www.speedlab.co.uk

Subject:

Date:

$$\text{iii) } P_{\text{MECH POWER}} = P_{\text{CAP}} (1-s)$$

$$\Rightarrow P_{\text{MECH}} = 2268 (1 - 0.1)$$

$$\Rightarrow P_{\text{MECH}} = \underline{\underline{2041 \text{ W}}}$$

$$\text{iv) } \text{TORQUE} = \frac{P_{\text{MECH}}}{\text{SPEED}} = \frac{2041}{\frac{1350 \times 2\pi}{60}} = \underline{\underline{14.4 \text{ Nm}}}$$

$$\text{v) } \text{IRON LOSS} = \frac{3V_{\text{PH}}^2}{k_c} = \frac{231^2 \times 3}{1500} = 35.5 \text{ W} \times 3 = \underline{\underline{107 \text{ W}}}$$

$$\text{STATOR COPPER LOSS} = 3I_r^2 R_s = 3 \times 3.55^2 \times 5 = \underline{\underline{189 \text{ W}}}$$

$$\text{ROTOR COPPER LOSS} = 3I_r^2 R_r = 3 \times 3.55^2 \times 6 = \underline{\underline{227 \text{ W}}}$$

$$\text{TOTAL POWER LOSS} = \underline{\underline{523 \text{ W}}}$$



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject: Date:

$$vi) \text{ INPUT POWER} = \text{OUTPUT POWER} + \text{LOSSES}$$

$$\Rightarrow \text{INPUT POWER} = 2041 + 523 = \underline{\underline{2564 \text{ W}}}$$

$$vii) \text{ EFFICIENCY} = \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \times 100\%$$

$$\Rightarrow \text{EFFICIENCY} = \frac{2041}{2564} \times 100\% = \underline{\underline{79.6\%}}$$

viii) FROM THE EQUIVALENT CIRCUIT:

$$\bar{I}_s = \bar{I}_m + \bar{I}_c + \bar{I}_r$$

So need to determine \bar{I}_m , \bar{I}_c & \bar{I}_r in
Cartesian Coordinates:

$$\bar{I}_m = \frac{\bar{V}_{ph}}{jX_m} = \frac{271 \angle 0^\circ}{400 \angle 90^\circ} = 0.58 \angle -90^\circ$$

$$\Rightarrow \bar{I}_m = -j 0.58$$



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject:

Date:

$$\bar{I}_c = \frac{\bar{V}_{an}}{R_c} = \frac{231 \angle 0^\circ}{1500 \angle 0^\circ} = 0.15$$

$$\bar{I}_c = 3.55 \angle -3.5^\circ \equiv 3.54 - j0.22$$


$$\Rightarrow \bar{I}_s = \bar{I}_m + \bar{I}_c + \bar{I}_a$$

$$\Rightarrow \bar{I}_s = -j0.58 + 0.15 + 3.54 - j0.22$$

$$\Rightarrow \bar{I}_s = 3.69 - j0.8$$

$$\Rightarrow \bar{I}_s = \underline{\underline{3.78 \angle -12.2^\circ}}$$

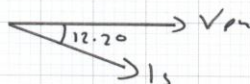Angle Between \bar{V}_{an} & \bar{I}_s is 12.2°




$$\Rightarrow \text{Power Factor} = \cos 12.2^\circ = \underline{\underline{0.977}}$$

(NOTE $3V_{an}I_s \cos \phi$ SHOULD EQUAL INPUT POWER!)

Subject: Date:

Q4

SIMPLIFIED EQUIVALENT CIRCUIT:

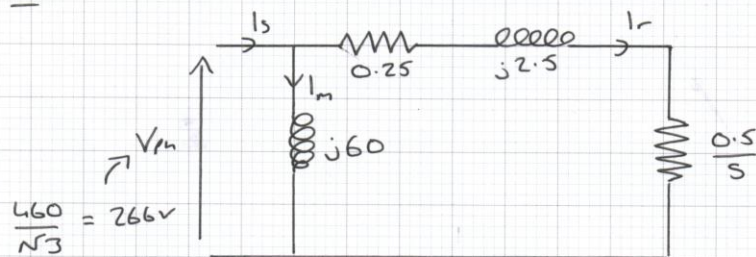

(No Iron Loss so R_c not included)

FIRST OF ALL CALCULATE I_m (this value is
 the same for both Standstill and Rated
 Speed operation)

$$\bar{I}_m = \frac{\bar{V}_{ph}}{jX_m} = \frac{266 \angle 0^\circ}{60 \angle 90^\circ} = \underline{\underline{4.43 \angle -90^\circ}}$$

STANDSTILL ($s = 1$)

$$\frac{R_r}{s} = \frac{0.5}{1} = 0.5$$

Subject:

Date:

$$Z_T = 0.25 + j2.5 + 0.5$$

$$\Rightarrow Z_T = 0.75 + j2.5 \equiv 2.61 \angle 73.3^\circ$$

$$\Rightarrow \bar{I}_r = \frac{\bar{V}_{oc}}{Z_T} = \frac{266 \angle 0^\circ}{2.61 \angle 73.3^\circ} = 102 \angle -73.3^\circ$$

$$\Rightarrow \bar{I}_r \equiv 29.3 - j97.7$$

$$\bar{I}_s = \bar{I}_m + \bar{I}_r = -j4.43 + 29.3 - j97.7$$

$$\Rightarrow \bar{I}_s = 29.3 - j102.1 \equiv \underline{\underline{106 \angle -74^\circ}}$$

AT RATED SPEED (1764 rpm)

$$N_s = \frac{120 \times 85}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

$$\Rightarrow S = \frac{N_s - N_r}{N_s} = \frac{1800 - 1764}{1800} = 0.02$$



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



12

Subject:

Date:

$$\Rightarrow \frac{R_r}{s} = \frac{0.5}{0.02} = \underline{\underline{25 \Omega}}$$

$$\Rightarrow Z_T = 0.25 + j2.5 + 25 = 25.25 + j2.5$$

$$\Rightarrow Z_T = 25.4 \angle 5.65^\circ$$

$$\Rightarrow \bar{I}_r = \frac{\bar{V}_{an}}{Z_T} = \frac{266 \angle 0^\circ}{25.4 \angle 5.65^\circ} = \underline{\underline{10.5 \angle -5.6^\circ}}$$

$$\Rightarrow \bar{I}_r = 10.4 - j1.03$$

$$I_s = \bar{I}_n + \bar{I}_r = -j4.43 + 10.4 - j1.03$$

$$\Rightarrow I_s = 10.4 - j5.5 = \underline{\underline{11.76 \angle -27.9^\circ}}$$

$$\text{Ratio: } \frac{\text{STARTING CURRENT}}{\text{FULL LOAD CURRENT}} = \frac{106}{11.76} = \underline{\underline{9.01}}$$

$$\text{FULL LOAD POWER FACTOR} = \cos(-27.9) = \underline{\underline{0.88}}$$

LAGGING

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157 Fax: +44(0)141 330 3158 Email: saffron@elec.gla.ac.uk Web: www.speedlab.co.uk