

Power Engineering 3

Tutorial 1 Solution



SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.




Subject: Power Eng 2: Tutorial 1 Date: _____

Q1. a) $V_{rms} = \frac{V_{pk}}{\sqrt{2}} = \frac{141}{\sqrt{2}} = \underline{\underline{99.7V}}$


b) $I_{rms} = \frac{I_{pk}}{\sqrt{2}} = \frac{20}{\sqrt{2}} = \underline{\underline{14.1A}}$

Q2.

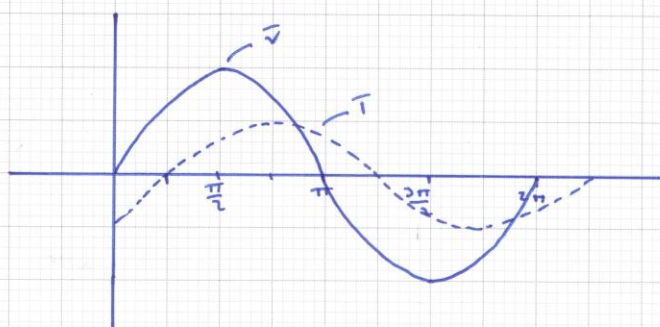

THE CURRENT LAGS THE VOLTAGE BY 45°

Q3.

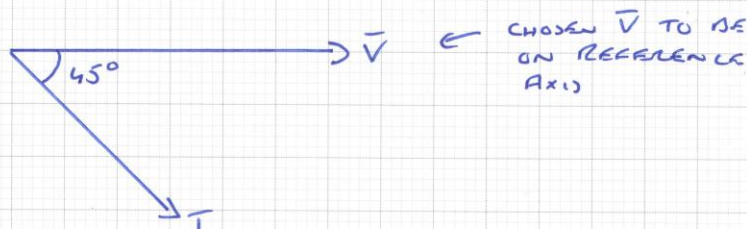



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



②

Subject:


Date:

Q4 a)



$$I_{rms} = \frac{V_{rms}}{R} = \frac{100}{5} = \underline{\underline{20A}}$$

b)

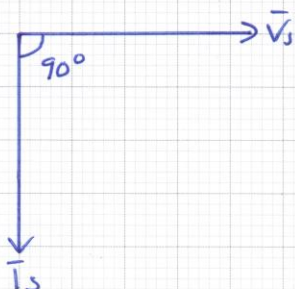


$$X_L = \omega L = 2\pi \times 50 \times 15 \times 10^{-3}$$

$$\Rightarrow X_L = 4.71 \Omega$$

$$I_{rms} = \frac{V_{rms}}{X_L} = \frac{240}{4.71} = \underline{\underline{50.9A}}$$

c)

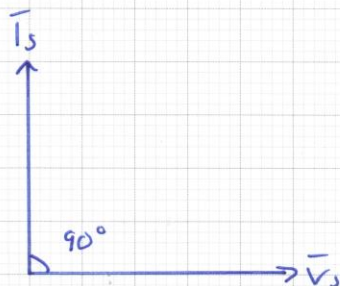

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 60 \times 3300 \times 10^{-6}}$$

$$\Rightarrow X_C = 0.8 \Omega$$

$$I_{rms} = \frac{V_{rms}}{X_C} = \frac{240}{0.8} = \underline{\underline{300A}}$$

Note: In each case we are computing MAGNITUDE only
of I_{rms} !

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject: Date:


Q5 $f = 60 \text{ Hz}$

a) $X_L = 2\pi f \times L = 6.28 \times 60 \times 220 \times 10^{-3}$
 $\Rightarrow X_L = \underline{\underline{82.9 \Omega}}$

b) $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 60 \times 220 \times 10^{-6}} = \underline{\underline{12.0 \Omega}}$

Q6 a) $15 + j10$

Draw the Impedance Triangle.

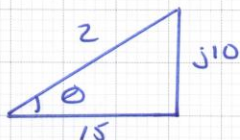

Note this has an
Inductive Element a
+j Component

$$Z^2 = (R^2 + X_L^2) = (15^2 + 10^2) = 325$$

$$\Rightarrow Z = 18 \Omega$$

$$\theta = \cos^{-1} \frac{15}{18} = 33.5^\circ \left(\begin{array}{l} \text{BETTER TO} \\ \text{USE} \\ \tan^{-1} \frac{10}{15} \end{array} ! \right)$$

$$\Rightarrow \underline{\underline{18 \angle 33.5^\circ}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk



UNIVERSITY
of
GLASGOW

SPEED Laboratory


To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject: Date:

Q6 b) $20 - j30$

Draw the Impedance Triangle:

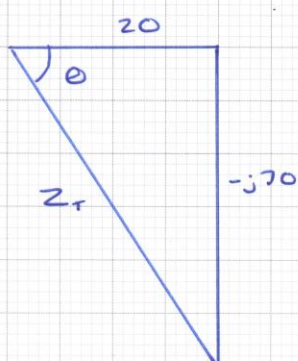

$$\begin{aligned} Z_r^2 &= (R^2 + X_c^2) \\ &= 20^2 + 30^2 \\ &= 1300 \end{aligned}$$

$$\Rightarrow Z_r = 36$$

$$\theta = \tan^{-1} \frac{-30}{20} = -56.3^\circ$$

(Note θ is -ve)

That's why drawing the Impedance Triangle is
worthwhile as we can clearly see θ is NEGATIVE

$$Z_c = \underline{\underline{36 \angle -56.2^\circ}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.




Subject:

Date:

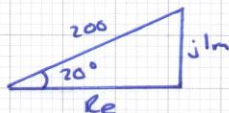Q7 a) $\bar{V} = 200 \angle 20^\circ$

Draw the Phasor on the Complex Plane
to Determine Real and Imaginary Parts:




$$\begin{aligned} \text{Re} &= H \cos \theta \\ &= 200 \cos 20^\circ = 188 \end{aligned}$$

$$\begin{aligned} \text{Im} &= H \sin \theta \\ &= 200 \sin 20^\circ = 68.4 \end{aligned}$$

$$\Rightarrow \bar{V} = \underline{\underline{188 + j68.4}}$$

b) $\bar{V} = 100 \angle -40^\circ$

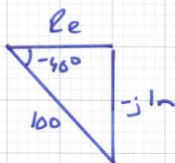

$$\begin{aligned} \text{Re} &= H \cos \theta \\ &= 100 \cos -40^\circ = 76.6 \end{aligned}$$

$$\begin{aligned} \text{Im} &= H \sin \theta \\ &= 100 \sin -40^\circ = -64.2 \end{aligned}$$

$$\Rightarrow \bar{V} = \underline{\underline{76.6 - j64.2}}$$



UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



6

Subject:

Date:

Q8 a) $X_L = \omega L$
 $\Rightarrow L = \frac{X_L}{\omega} = \frac{20}{2\pi \times 50} = \underline{\underline{63.7 \text{ nH}}}$


b) $\bar{V}_s = Z_T \bar{I}_s$
 $\Rightarrow \bar{I}_s = \frac{\bar{V}_s}{Z_T}$

Need to determine Polar value for Z_T :

$$Z_T = 15 + j20$$

$$Z^2 = (15^2 + 20^2) = 625$$
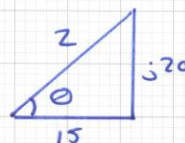
$$\Rightarrow Z = \underline{\underline{25}}$$



$$\cos \theta = \frac{A}{H} = \frac{15}{25} = 0.6$$

(Better to use $\tan^{-1} \frac{20}{15}$!)

$$\Rightarrow \theta = 53.1^\circ \quad \Rightarrow Z_T = \underline{\underline{25 \angle 53.1^\circ}}$$

$$\Rightarrow \bar{I}_s = \frac{\bar{V}_s}{Z_T} = \frac{110 \angle 0^\circ}{25 \angle 53.1^\circ} = \underline{\underline{4.4 \angle -53.1^\circ}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk



UNIVERSITY
of
GLASGOW


SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject:

Date:

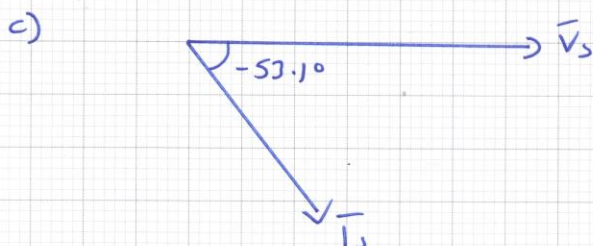

$$d) P_{out} = I_s^2 R = 4.4^2 \cdot 15 = \underline{\underline{290 \text{ W}}}$$

$$e) \text{ Input Power} = \text{Total Output Power}$$

$$\Rightarrow P_{in} = \underline{\underline{290 \text{ W}}}$$

$$f) \bar{V}_R = L \cdot \bar{I}_s = 15 \cdot 4.4 \angle -53.1^\circ$$

$$\Rightarrow \bar{V}_R = \underline{\underline{66 \angle -53.1^\circ}}$$

$$\bar{V}_L = Z_L \bar{I}_s = j20 \cdot 4.4 \angle -53.1^\circ$$

$$= 20 \angle 90^\circ \cdot 4.4 \angle -53.1^\circ$$

$$= \underline{\underline{88 \angle 36.9^\circ}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk




UNIVERSITY
of
GLASGOW

SPEED Laboratory

To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject: Date:

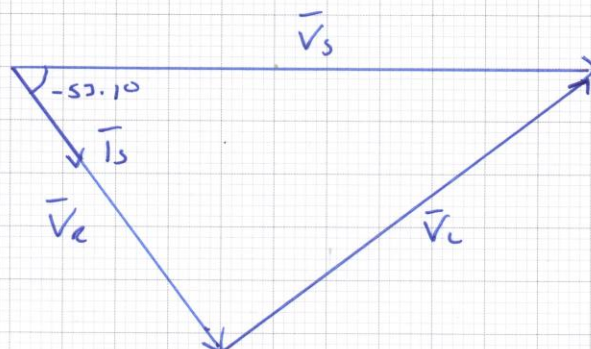


Q9

a) $Z_T = j10 + 5 - j20 = \underline{\underline{5 - j10}}$

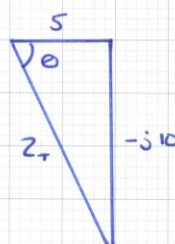b) $\bar{I}_s = \frac{\bar{V}_s}{Z_T}$

$\Rightarrow \bar{I}_s = \frac{11000 \angle 0^\circ}{11.18 \angle -67.4^\circ}$

$\Rightarrow \bar{I}_s = \underline{\underline{987.4 \angle 67.4^\circ}}$



$Z_T^2 = 5^2 + 10^2$
 $= 125$

$\Rightarrow Z_T = 11.18$

$\theta = \tan^{-1} \frac{-10}{5}$

$\Rightarrow \theta = -67.4^\circ$

$\Rightarrow Z_T = 11.18 \angle -67.4^\circ$



UNIVERSITY
of
GLASGOW

SPEED Laboratory


To serve industry with the most advanced CAD software
for electric motors and drives,
supported by special control hardware and test equipment,
with consultancy, long-term research, and education.



Subject:

Date:

c)

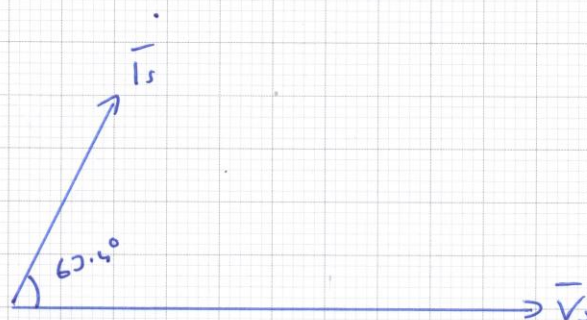

d) For the current to be in phase with the voltage then the imaginary part must equal zero so Z_T

$$\Rightarrow Z_T = R + j0$$

$$\Rightarrow Z_T = R + j10 - j10$$

\uparrow
 Z_L

\downarrow
 Z_C

$$\Rightarrow Z_C = -j10$$

$$\Rightarrow X_C = 10 = \frac{1}{\omega C}$$

$$\Rightarrow C = \frac{1}{10\omega} = \frac{1}{10 \cdot 2\pi \times 50} = \underline{\underline{318 \mu F}}$$

Department of Electronics & Electrical Engineering, University of Glasgow, Rankine Building, Oakfield Avenue, Glasgow G12 8LT, UK

Tel: +44 (0)141 330 3157

Fax: +44(0)141 330 3158

Email: saffron@elec.gla.ac.uk

Web: www.speedlab.co.uk