



POWER ENGINEERING
#03 SINGLE-PHASE AC POWER SYSTEMS
AC CIRCUIT ANALYSIS

2018



University
of Glasgow

Today we will investigate:

- Components of a simple Electrical Power System
- AC Voltage Source:
 - Instantaneous Voltage
 - Average & RMS Voltage
- Phasor Diagram Representation
- Resistive, Inductive and Capacitive loads:
 - Voltage v Current relationship
 - Impedance & Reactance
- Complex Loads (combination of R, L and C components)

A Simple Electrical Power System:

**Electrical
Generator**



**Electrical
Transformer**



Electrical Loads



lighting




heating



motors

Each of these components can be represented by an equivalent circuit made up of a combination of simple electrical components: voltage source, resistance, inductance and capacitance

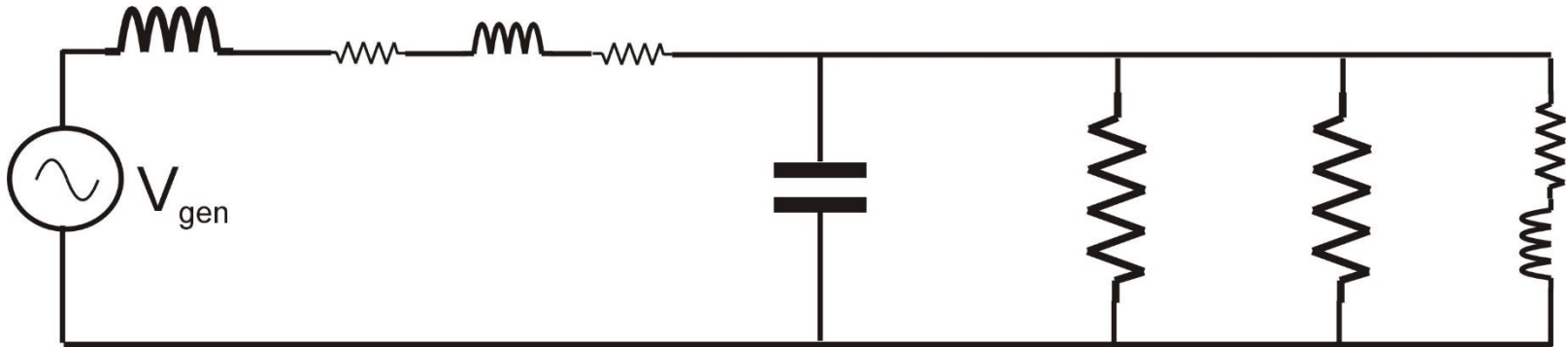A Simple Electrical Power System (Equivalent Circuit):




Once we have the equivalent circuit we can determine component voltages and currents, and then from this determine **POWER** related properties such as Real Power, Apparent Power, System Efficiency and Power Factor (we'll talk about these in detail on Thursday)

Before we move onto analysing equivalent circuits let's have a brief look at the properties of each circuit component

ELECTRICAL CIRCUIT

To have an electrical circuit with flowing current, we need

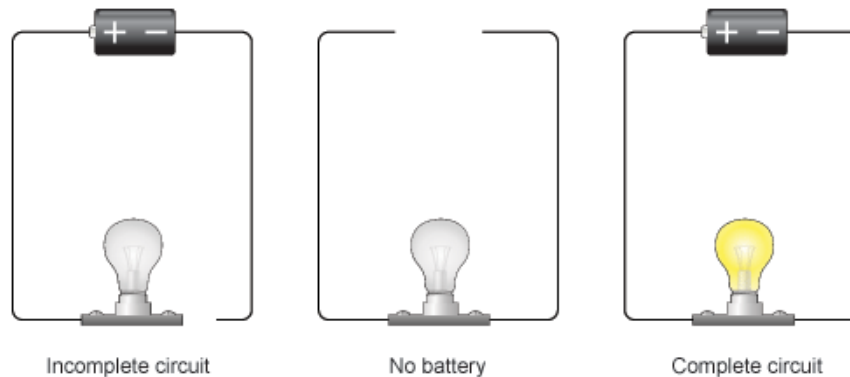- (Power) Source 电源 : Voltage Source, Current Source, Dependant (Controlled) Source
- Complete (闭合) paths formed by conductors and components (Resistor, Inductor, Capacitor)



The bulb will only light if there is a battery and a complete circuit

We usually add in a **switch** (开关) to the circuit, so that we can break (关断) the circuit and stop (阻断) the electric current when we want to.

LINEAR ELECTRICAL CIRCUIT 线性电路

An equivalent definition of a linear circuit is that it obeys the **Superposition Principle** (叠加原理) in steady states. When a linear combination of signals $\mathbf{a}\mathbf{x}_1(t) + \mathbf{b}\mathbf{x}_2(t)$ is applied to a linear circuit $\mathbf{F}(\mathbf{x})$, the output of $\mathbf{F}(\mathbf{x})$ is equal to the linear combination of the outputs due to the signals $\mathbf{x}_1(t)$ and $\mathbf{x}_2(t)$ applied separately:

$$F(a \cdot X_1(t)) = a \cdot F(X_1(t))$$

$$F(b \cdot X_2(t)) = b \cdot F(X_2(t))$$

$$F(a \cdot X_1(t) + b \cdot X_2(t)) = a \cdot F(X_1(t)) + b \cdot F(X_2(t))$$

Linear circuits are important because they can process analogue signals without introducing intermodulation distortion. This means that **separate frequencies in the signal stay separate and do not mix, creating new frequencies**. It is easy to analyse linear circuits using many mathematical techniques, e.g. Fourier analysis, Laplace Transform in frequency domain (频域) .

LINEAR ELECTRICAL CIRCUIT

A linear circuit is an electronic circuit in which, for a sinusoidal input voltage of frequency f , any steady-state output of the circuit (the current through any component, or the voltage between any two points) is also sinusoidal with frequency f . Note: a dc signal can also be treated as a sinusoidal input voltage of frequency $f=0$.

A linear circuit has no nonlinear electronic components in it.

- Examples of linear circuits are amplifiers 比例放大器, differentiators 微分器, and integrators 积分电路, or any circuit composed exclusively of ideal passive 无源的 LCR (resistors, capacitors, inductors), active 有源的 op-amps (in the “non-saturated 不饱和” regime), and other “linear” elements.
- Some examples of nonlinear (非线性) electronic components are: diodes, transistors, and inductors and transformers when the iron core is saturated, digital logic circuit, etc.

Resistive Elements

Examples:

- General Wiring
- Resistive loads (lighting, heating)
- Dump Resistors in power converters



Electrical Symbol



SI Units

Ohm
(Ω)


Typical Values

m Ω - k Ω

Inductive Elements

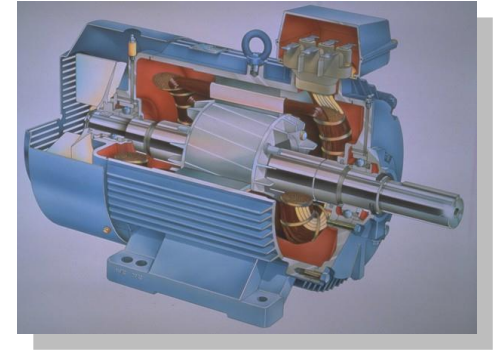Examples:

- General Wiring (stray inductance)
- Magnetic Components (Transformers, Electric Motors)
- Filters



Electrical Symbol



SI Units

**Henry
(H)**

Typical Values

μH - mH

Capacitive Elements

Examples:

- General Wiring (stray capacitance)
- Power Factor Correction
- Filters



Electrical Symbol



SI Units

Farad (F)

Typical Values

μF – 1000's μF






BASIC INDEPENDENT SOURCES

Voltage source

- Source of electrical potential difference. Voltage across it is independent of the current through it.

Current source

- Source of flow of electric charge. Current through it is independent of the voltage across it.

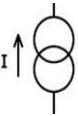	DC	AC
Voltage Source	 or 	
Current Source	 or 	

AC / DC

AC: flow of electrical charge alternates periodically



DC: flow of electrical charge is one direction & constant



BEHAVIOR OF BASIC PASSIVE (无源) ELEMENTS LCR



resistance (R) / conductance (G)
unit: ohm (Ω) / siemens (S)
Energy Dissipation Element
耗能元件



inductance (L)
unit: henry (H)
Energy Storage Element
储能元件

capacitance (C)
unit: farad (F)
Energy Storage Element
储能元件



Voltage-Current Relationship in Time Domain

	DC	AC
Resistor	$V = RI$ 欧姆定律	$v(t) = Ri(t)$
Inductor		$v(t) = L \frac{di(t)}{dt}$
Capacitor		$v(t) = \frac{1}{C} \int i(t) dt$

LCR元件时域特性

TECHNIQUES FOR LINEAR CIRCUIT ANALYSIS


Current Node method 电流节点法 and Voltage Mesh (Loop) method 电压网格/回路法

- Kirchhoff's Current Law (KCL) 基氏电流定律

$$\text{KCL: } \sum_k i_k = 0, \text{ for any node}$$

- Kirchhoff's Voltage Law (KVL) 基氏电压定律
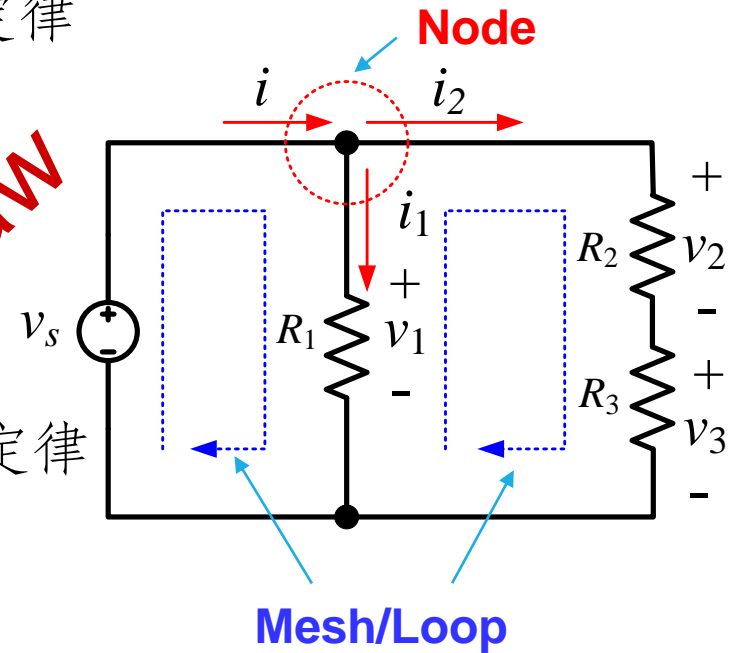
$$\text{KVL: } \sum_k v_k = 0, \text{ for any loop}$$




STEADY-STATE AND TRANSIENT RESPONSES

Steady state (稳态) is an equilibrium (平衡) condition of a circuit or network that occurs as the effects of transients are no longer important.

- All power waveforms repeat unchanged cyclically with fixed AC inputs when $t \rightarrow \infty$;
- All power waveforms keep unchanged with constant DC inputs when $t \rightarrow \infty$.

Transient response (瞬态) is to describe the behaviour of a power variable (voltage or current) during the transition between two distinct steady-state (equilibrium) conditions

STEADY-STATE ANALYSIS OF AC CIRCUIT

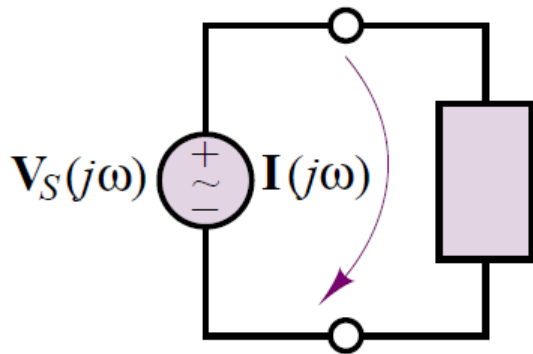

What's AC Circuit ?



- Circuit in Steady State;
- **Excitation Source V_s or I** is a sinusoidal function with constant *amplitude* and constant *frequency*.

DC Circuit Analysis actually can be treated as a special case of steady-state AC Circuit Analysis in the case of frequency $\omega=0$

Note: Steady State \neq DC

Ideal Voltage Source:

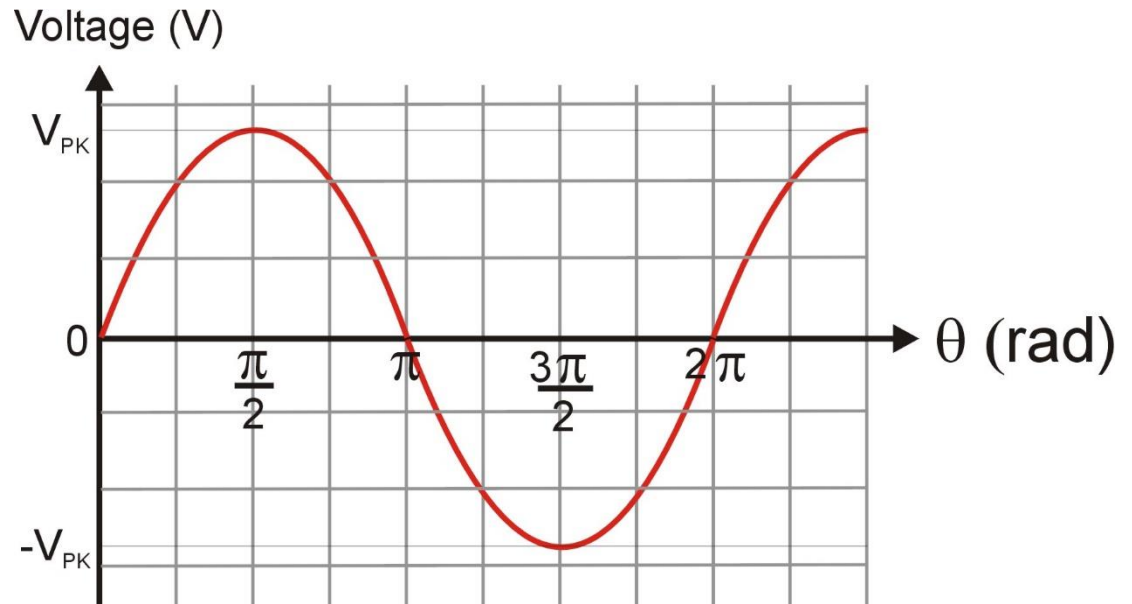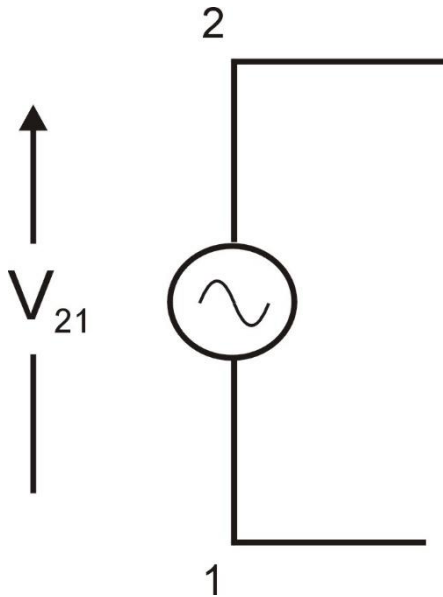Ideal means that the sinusoidal voltage does NOT change when a load is applied across its terminals



Expressions for Instantaneous Voltage: $v(\theta) = V_{PK} \sin \theta$

Example: 50Hz AC voltage


$$\omega = 2\pi \cdot f$$

$$\omega = 2\pi \cdot 50 = 314 \text{ rad/sec}$$

$$v(t) = V_{PK} \sin(\omega t)$$

Where ω = Voltage frequency in rad/sec

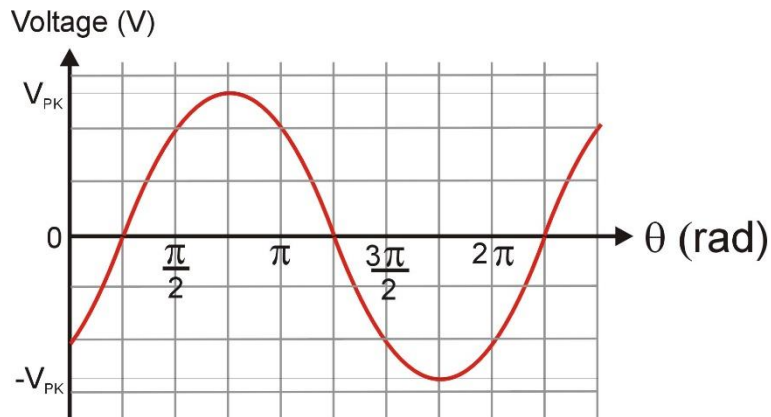
Note: the time/angle reference for the previous voltage waveform has been chosen to (arbitrarily) start at time/angle = 0, here are a couple of other examples where this is not the case:



$$v(\theta) = V_{PK} \sin\left(\theta - \frac{\pi}{4}\right)$$

$$v(t) = V_{PK} \sin\left(\omega t - \frac{\pi}{4}\right)$$

Phase Shift = -π/4 (delay)

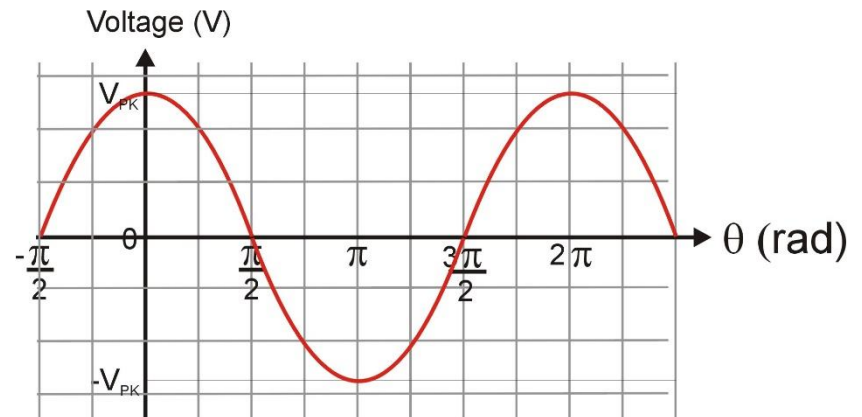

$$v(\theta) = V_{PK} \sin\left(\theta + \frac{\pi}{2}\right)$$

$$v(t) = V_{PK} \sin\left(\omega t + \frac{\pi}{2}\right)$$

Phase Shift = +π/2 (advance)

In time domain, it is quite easy to do DC circuit Analysis by using Ohm's Law

$$R = \frac{V}{I}$$

However, in time domain, AC circuit analysis with real number involves complicated calculus (differential equations) of trigonometric function. It is not easy !!!


How to simplify AC Circuit ANALYSIS ???

***Solving AC Circuits with Complex
Number !!!***

***Create mathematical tools – phasor &
impedance***

工欲善其事，必先利其器

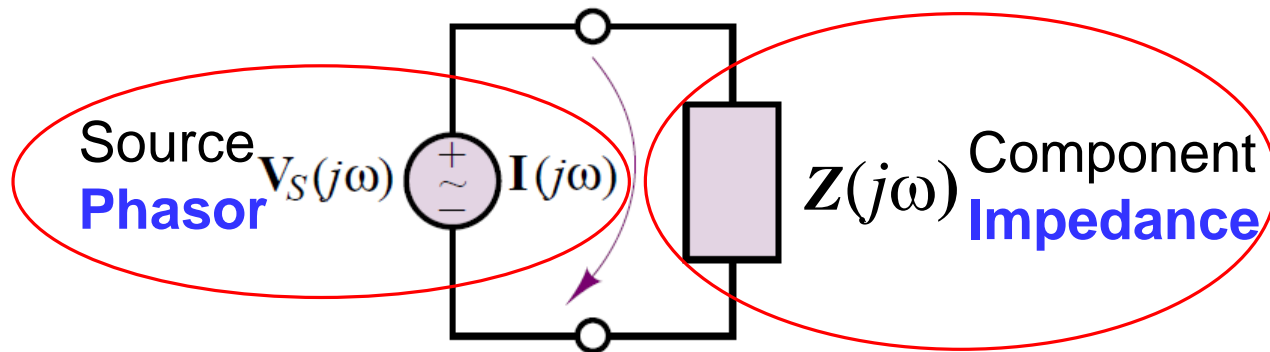STEADY-STATE ANALYSIS OF AC CIRCUIT WITH COMPLEX NOTATION – PHASOR & IMPEDANCE



The principal difference between a resistive circuit and an AC circuit is that the latter is frequency-dependent.

A GENERALISED SINUSOID CAN BE EXPRESSED AS THE REAL PART OF A COMPLEX VECTOR

$$\begin{aligned} v &= V_m \cos(\omega t + \phi) = \operatorname{Re} [V_m \cos(\omega t + \phi) + jV_m \sin(\omega t + \phi)] \\ &= \operatorname{Re} [V_m e^{j(\omega t + \phi)}] = \operatorname{Re} [\color{red}{V}_m \color{red}{e}^{j\phi} e^{j\omega t}] = \cancel{\operatorname{Re} [\color{red}{V} \color{blue}{e}^{j\omega t}]} \end{aligned}$$

PHASOR REPRESENTATION OF THE GIVEN SINUSOIDAL FUNCTION CAN BE DEFINED (SIMPLIFIED) AS

$$\color{red}{V}(j\omega) = \color{red}{V} = V_m e^{j\phi} \equiv V_m \angle \phi$$

where $\color{red}{V}(j\omega)$ or $\color{red}{V}$ is "the phasor of $\cos(\omega t + \Phi)$ ", the $j\omega$ indicating the $e^{j\omega t}$ dependence of the phasor (or the representation in frequency domain).

PHASOR (相量)

Any sinusoidal signal may be mathematically represented in one of two ways:

❑ time-domain form: $v(t) = A\cos(\omega t + \phi)$

❑ frequency-domain (or phasor) form: $\mathbf{V}(j\omega) = Ae^{j\phi} = A\angle\phi$


Note $j\omega$ in the notation $\mathbf{V}(j\omega)$, indicating $e^{j\omega t}$ dependence of the phasor.

Note:

- For a given frequency ω , *Phasor is only used to express sinusoidal voltage or current variables with complex number !!!*
- Phasors replaces time-varying sinusoidal functions with **constant complex numbers**, significantly simplify AC circuit analysis.
- *Simply Mathematical Convenience. No Real Physical Significance.*

PHASOR

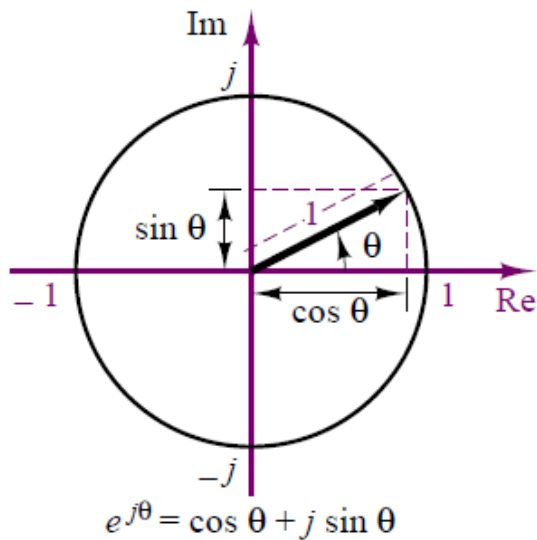The phasor concept is rooted in Euler's identity 欧拉等式, which relates the exponential function to the trigonometric function:



$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$\cos \theta = \operatorname{Re} [e^{j\theta}]$$

$$\sin \theta = \operatorname{Im} [e^{j\theta}]$$

$$|e^{j\theta}| = |\cos \theta + j \sin \theta| = \sqrt{\cos^2 \theta + \sin^2 \theta} = 1$$


PHASOR

$$\mathbf{V} = V_m e^{j\phi} \equiv V_m \angle \phi$$

V_m - magnitude (modulus 模)
 Φ - phase angle

Is a **complex number**.

$$\begin{array}{ccc} \text{Polar form} & \text{Exponential form} & \text{Rectangular form} \\ \mathbf{V} = |\mathbf{V}| \angle \Phi & = |\mathbf{V}| e^{j\Phi} & = |\mathbf{V}| (\cos \Phi + j \sin \Phi) \\ |\mathbf{V}| = V_m & & \end{array}$$

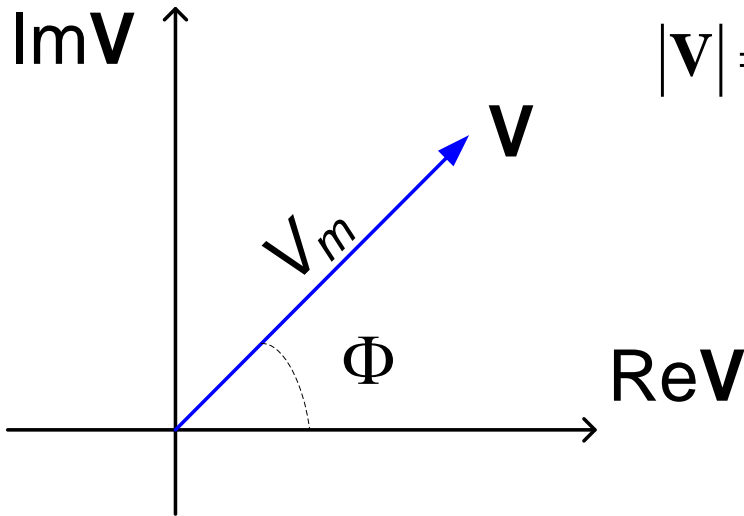


The **phasor** is a complex number that carries the **amplitude** and **phase angle** information of a **sinusoidal function**.

Phasor Diagram representation of Voltages (and Currents):


It is rather time consuming to draw sinusoidal waveforms, a quicker way of representing voltages and currents in the form of a *PHASOR*. The phasor diagram very quickly illustrates:

- 1] The RMS magnitude (see later slide for definition) of the voltage (length of the phasor)
- 2] The phase of the voltage (the angle of the phasor wrt a Reference (0°) axis)

Phasor Diagram:

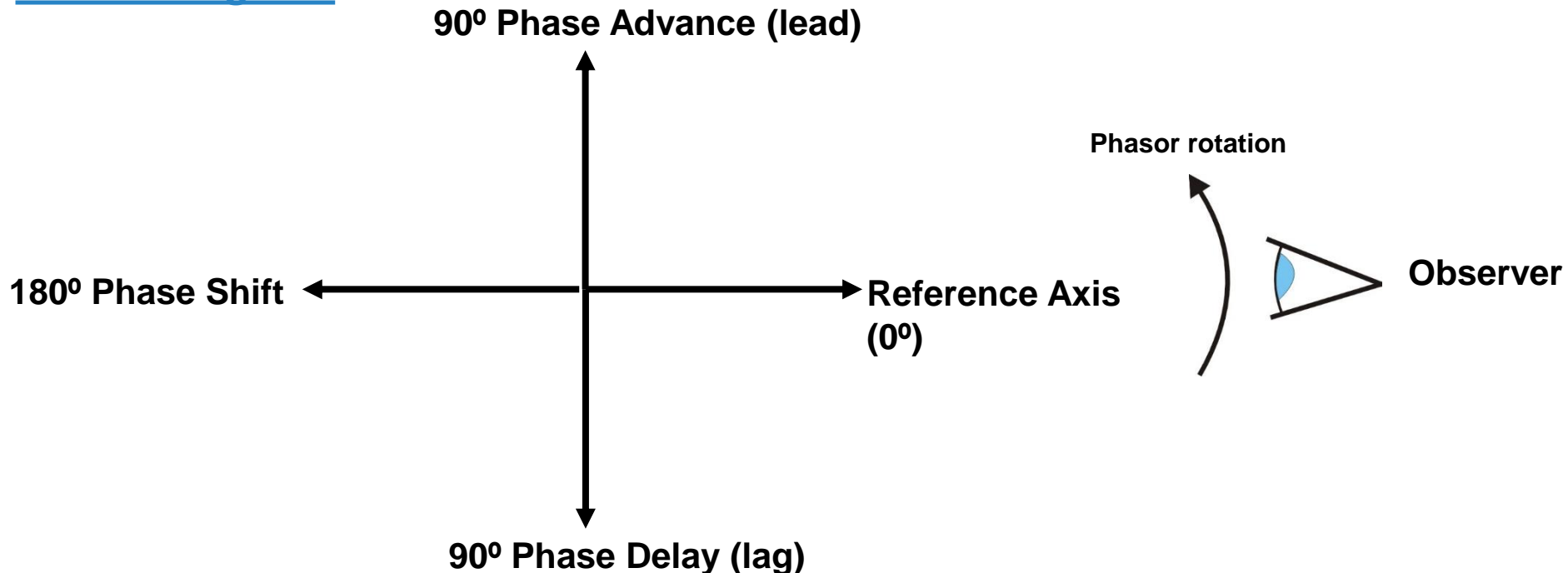

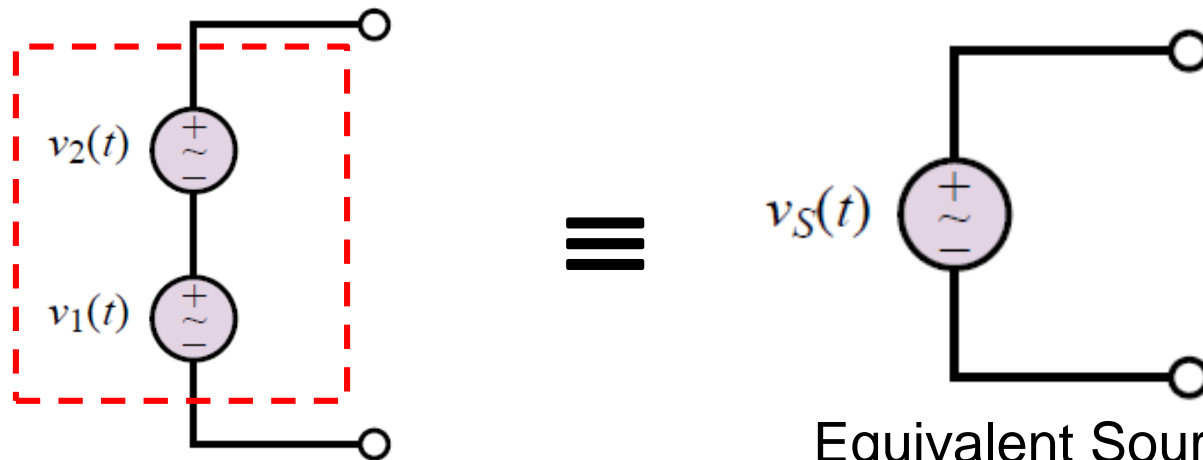EXAMPLE — *ADDITION OF TWO SINUSOIDAL SOURCES IN PHASOR NOTATION*



$$v_1(t) = 15 \cos(377t + \pi/4) \text{ V}$$

$$v_2(t) = 15 \cos(377t + \pi/12) \text{ V}$$

Equivalent Source

$$v_S(t) = v_1(t) + v_2(t)$$

Note: $v_1(t)$ and $v_2(t)$ are sinusoids with identical frequency

Time Domain Form : $v_1(t) = 15 \cos(377t + \pi/4) \text{ V}$
 $v_2(t) = 15 \cos(377t + \pi/12) \text{ V}$

Polar Form Phasor : $\mathbf{V}_1(j\omega) = 15\angle\pi/4 \text{ V}$
 $\mathbf{V}_2(j\omega) = 15e^{j\pi/12} = 15\angle\pi/12 \text{ V}$

Rectangular Form : $\mathbf{V}_1(j\omega) = 10.61 + j10.61 \text{ V}$
 Phasor : $\mathbf{V}_2(j\omega) = 14.49 + j3.88$

Equivalent Voltage Phasor:

$$\mathbf{V}_S(j\omega) = \mathbf{V}_1(j\omega) + \mathbf{V}_2(j\omega) = 25.10 + j14.49 = 28.98e^{j\pi/6} = 28.98\angle\pi/6 \text{ V}$$

Convert $\mathbf{V}_S(j\omega)$ to its time domain form:

$$v_S(t) = 28.98 \cos(377t + \pi/6) \text{ V}$$

IMPEDANCE (阻抗) :

“A GENERALISED *COMPLEX RESISTANCE*”

Impedance: *i-v relationship* of three idea circuit elements **LCR** are described using complex number (frequency domain) in light of Voltage Phasor and Current Phasor

$$\mathbf{Z}(j\omega) = \mathbf{V}(j\omega) / \mathbf{I}(j\omega)$$


Note: *Impedance is just a complex number, but not a Phasor*

!!!

IMPEDANCE OF A RESISTOR

Ohm's Law: i - v relationship of Resistor
in time domain

$$v(t) = i(t)R$$

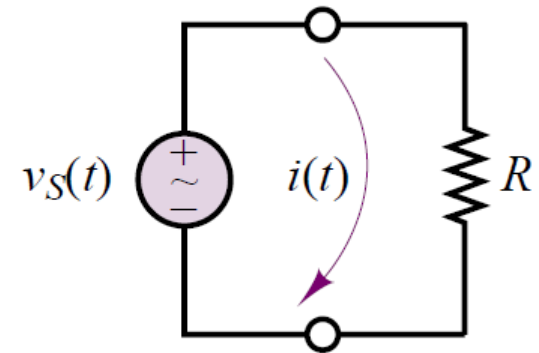

$$\therefore v_S(t) = V_m \cos(\omega t + \theta) \quad \text{or} \quad \mathbf{V}_S = V_m e^{j\theta} = V_m \angle \theta \quad \text{Voltage Phasor}$$


$$\Rightarrow i(t) = \frac{V_m}{R} \cos(\omega t + \theta) \quad \text{or} \quad \mathbf{I} = \frac{V_m}{R} e^{j\theta} = \frac{V_m}{R} \angle \theta \quad \text{Current Phasor}$$

$$Z_R(j\omega) = \frac{\mathbf{V}_S(j\omega)}{\mathbf{I}(j\omega)} = R \quad \text{Impedance of a resistor}$$

IMPEDANCE OF AN INDUCTOR

i - v relationship of
Inductor in time domain:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

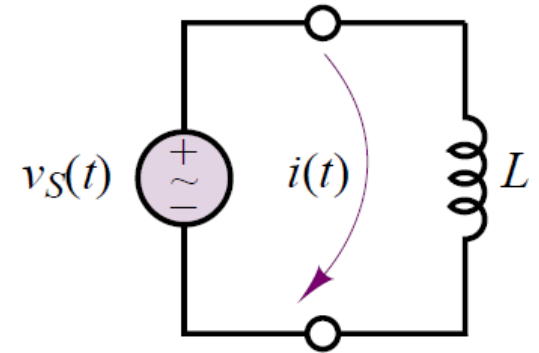


$$\because v_S(t) = V_m \cos(\omega t + \theta) \quad \text{or} \quad \mathbf{V}_S = V_m e^{j\theta} = V_m \angle \theta \quad \text{Voltage Phasor}$$

$$\Rightarrow i(t) = \frac{1}{L} \int V_m \cos(\omega t + \theta) dt = \frac{V_m}{\omega L} \sin(\omega t + \theta) = \frac{V_m}{\omega L} \cos\left(\omega t + \theta - \frac{\pi}{2}\right) \quad \text{or}$$

$$\mathbf{I} = \frac{V_m}{\omega L} e^{j\left(\theta - \frac{\pi}{2}\right)} = \frac{V_m}{\omega L} \angle \left(\theta - \frac{\pi}{2}\right) \quad \text{Current Phasor}$$
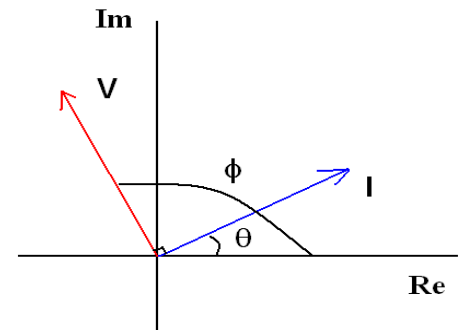
$$Z_L(j\omega) = \frac{\mathbf{V}_S(j\omega)}{\mathbf{I}(j\omega)} = \omega L \angle \pi/2 = j\omega L \quad \text{Impedance of an inductor}$$




Note: $j = e^{j\frac{\pi}{2}} = \angle \frac{\pi}{2} = \cos 90^\circ + j \sin 90^\circ$

IMPEDANCE OF A CAPACITOR

***i-v* relationship** of
Capacitor in time domain:

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

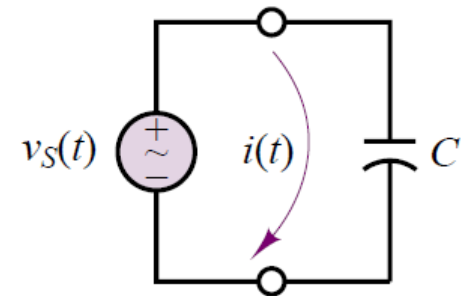

$\because v_S(t) = V_m \cos(\omega t + \theta)$ or $\mathbf{V}_S = V_m e^{j\theta} = V_m \angle \theta$ **Voltage Phasor** AC circuits


$$\Rightarrow i(t) = C \frac{d[V_m \cos(\omega t + \theta)]}{dt} = -\omega C V_m \sin(\omega t + \theta) = \omega C V_m \cos\left(\omega t + \theta + \frac{\pi}{2}\right) \text{ or}$$

$$\mathbf{I} = \omega C V_m e^{j\left(\theta + \frac{\pi}{2}\right)} = \omega C V_m \angle \left(\theta + \frac{\pi}{2}\right) \text{ **Current Phasor**}$$

$$\begin{aligned} Z_C(j\omega) &= \frac{\mathbf{V}_S(j\omega)}{\mathbf{I}(j\omega)} = \frac{1}{\omega C} \angle -\pi/2 \\ &= \frac{-j}{\omega C} = \frac{1}{j\omega C} \end{aligned} \quad \text{Impedance of a capacitor}$$

Not
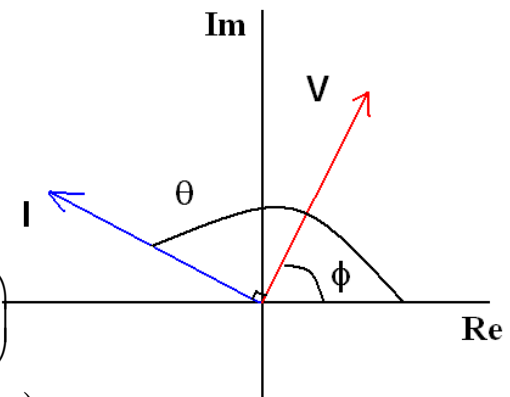
$$\begin{aligned} \underline{\underline{j}} &= \frac{1}{j} = e^{-j\frac{\pi}{2}} = \angle \left(-\frac{\pi}{2}\right) \\ &= \cos(-90^\circ) + j \sin(-90^\circ) \end{aligned}$$



IMPEDANCE IN AC CIRCUIT ANALYSIS


– GENERISED COMPLEX “*RESISTANCE*” OF LCR

Generic “AC Ohm’s Law”: $\mathbf{V} = \mathbf{ZI}$,

$$Z_R(j\omega) = \frac{\mathbf{V}_S(j\omega)}{\mathbf{I}(j\omega)} = R \quad \text{Impedance of a resistor}$$

$$Z_L(j\omega) = \frac{\mathbf{V}_S(j\omega)}{\mathbf{I}(j\omega)} = \omega L \angle \pi/2 = j\omega L \quad \text{Impedance of an inductor}$$
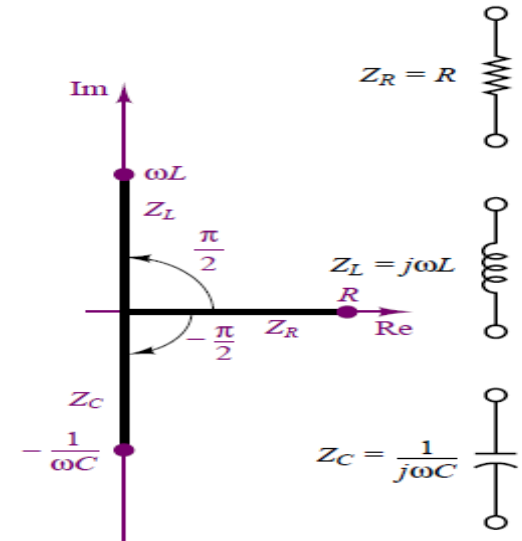
$$\begin{aligned} Z_C(j\omega) &= \frac{\mathbf{V}_S(j\omega)}{\mathbf{I}(j\omega)} = \frac{1}{\omega C} \angle -\pi/2 \\ &= \frac{-j}{\omega C} = \frac{1}{j\omega C} \end{aligned} \quad \text{Impedance of a capacitor}$$



$$e^{j\frac{\pi}{2}} = e^{j90^\circ} = \cos 90^\circ + j \sin 90^\circ = j$$


Impedance of LCR

Component	Voltage/Current Phase Relationship	Complex Impedance (Cartesian)	Complex Impedance (Polar)
Resistance	Voltage and Current are in phase	$Z_R = R + j0$	$Z_R = R \angle 0^\circ$
Inductance	Current lags the Voltage by 90°	$Z_L = 0 + j\omega L$	$Z_L = \omega L \angle 90^\circ$
Capacitance	Current leads the Voltage by 90°	$Z_C = 0 - j/\omega C$	$Z_C = \frac{1}{\omega C} \angle -90^\circ$

Note The REACTANCE (X_L) of an Inductance = ωL and the REACTANCE (X_C) of a capacitance = $1/\omega C$

GENERIC COMPONENT IMPEDANCE

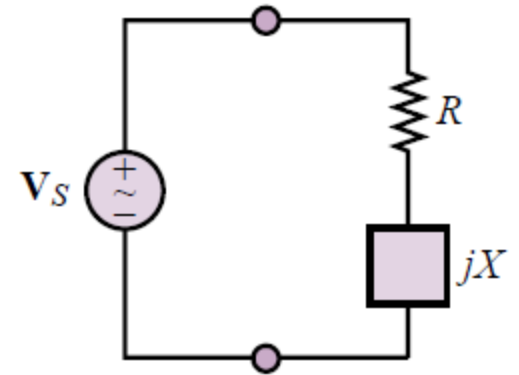Generic component Impedance represents the **equivalent impedance** of a combination of LCR components



Impedance $Z = R + jX$


阻抗 (resistance) \uparrow reactance

$\frac{1}{Z} = Y = G + jB$

电导 (conductance) \uparrow susceptance

导纳 (admittance) \uparrow 电纳

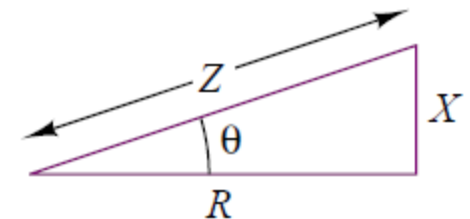$Z = R$ $j\omega L$ $\frac{1}{j\omega C} = \frac{-j}{\omega C}$



Impedance Triangle

Impedance enables AC circuits to be analysed in the same way as DC ~~an~~ circuits, but with complex numbers.

BASIC OPERATIONS $+$ $-$ \times \div OF COMPLEX NUMBER

$$\mathbf{Z} = R + jX = |Z| \angle \varphi, \quad |Z| = \sqrt{R^2 + X^2}, \quad \varphi = \arctan(X/R), \quad R = |Z| \cos(\varphi) \quad X = |Z| \sin(\varphi)$$

Conjugate $\mathbf{Z}^* = R - jX, \quad ZZ^* = |Z|^2 = (R + jX)(R - jX) = R^2 + X^2, \quad j^2 = -1$

$|Z|$ - magnitude (modulus 模), φ - phase angle

$$\mathbf{Z}_1 = a + jb = |Z_1| \angle \varphi_1, \quad \mathbf{Z}_2 = c + jd = |Z_2| \angle \varphi_2$$

$$\mathbf{Z}_1 \pm \mathbf{Z}_2 = (a \pm c) + j(b \pm d) = (|Z_1| \cos \varphi_1 \pm |Z_2| \cos \varphi_2) + j(|Z_1| \sin \varphi_1 \pm |Z_2| \sin \varphi_2)$$

$$\mathbf{Z}_1 \mathbf{Z}_2 = (a + jb)(c + jd) = (ac - bd) + j(ad + bc) = |Z_1| |Z_2| \angle (\varphi_1 + \varphi_2)$$

$$\begin{aligned} \mathbf{Z}_1 / \mathbf{Z}_2 &= (a + jb) / (c + jd) = [(a + jb)(c - jd)] / (c^2 + d^2) \\ &= [(ac + bd) + j(bc - ad)] / (c^2 + d^2) = (|Z_1| / |Z_2|) \angle (\varphi_1 - \varphi_2) \end{aligned}$$

IMPEDANCE ENABLES AC CIRCUITS TO BE ANALYZED IN THE SAME WAY AS DC (“**RESISTIVE**”) CIRCUITS, BUT WITH **COMPLEX NUMBERS**

Resistor

Series Resistance

$$R_{eq} = \sum_{s=1}^S R_s$$

Parallel Resistance

$$R_{eq} = \left[\sum_{p=1}^P \frac{1}{R_p} \right]^{-1}$$



Impedance

Series Impedance

$$Z_{eq} = \sum_{s=1}^S Z_s = Z_1 + Z_2 + \dots + Z_S$$

Parallel Impedance
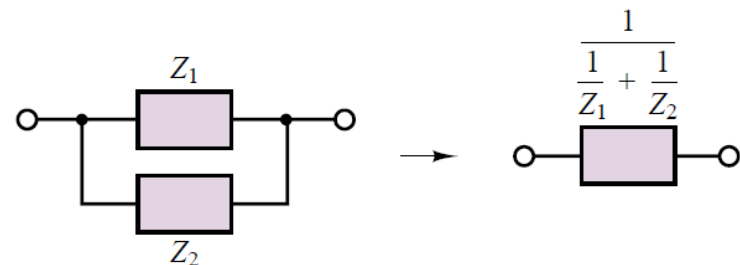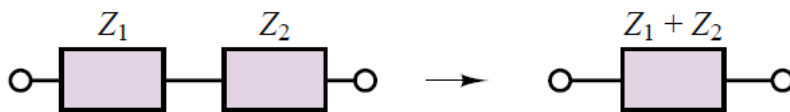
$$Z_{eq} = \left[\sum_{p=1}^P \frac{1}{Z_p} \right]^{-1} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_P}}$$



ADMITTANCE 导纳

For the analysis of certain circuits, such as circuits with many parallel elements, it is more easily to be handled in terms of Admittance Y . Just as the *reciprocal* (倒数) conductance (电导) $G=1/R$ of a resistive element R in DC circuit analysis, Admittance Y is defined as the inverse of Impedance Z in AC circuit analysis.



$I = Y V$ ($Y = 1/Z$), where Y is **admittance** of the component


$$\text{Resistor: } Y_R = 1/R = G \quad G \angle 0^\circ$$

$$\text{Capacitor: } Y_C = j\omega C \quad \omega C \angle 90^\circ$$

$$\text{Inductor: } Y_L = -j/(\omega L) \quad 1/\omega L \angle -90^\circ$$

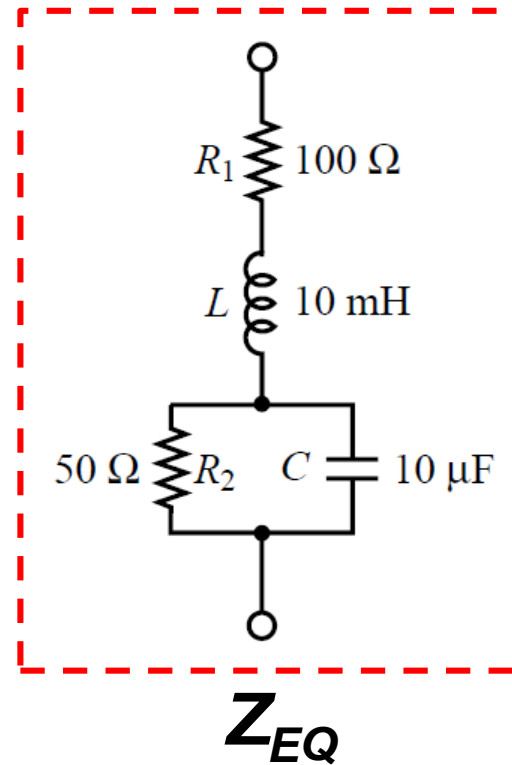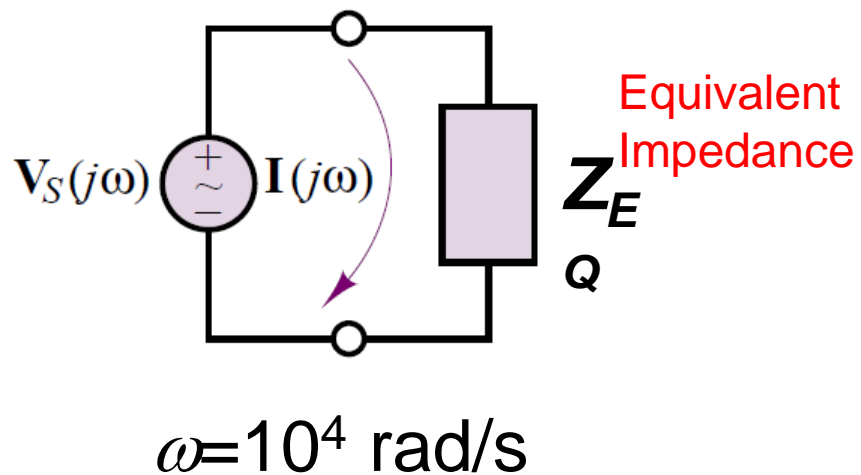EXAMPLE — *IMPEDANCE OF A GENERIC COMPONENT*



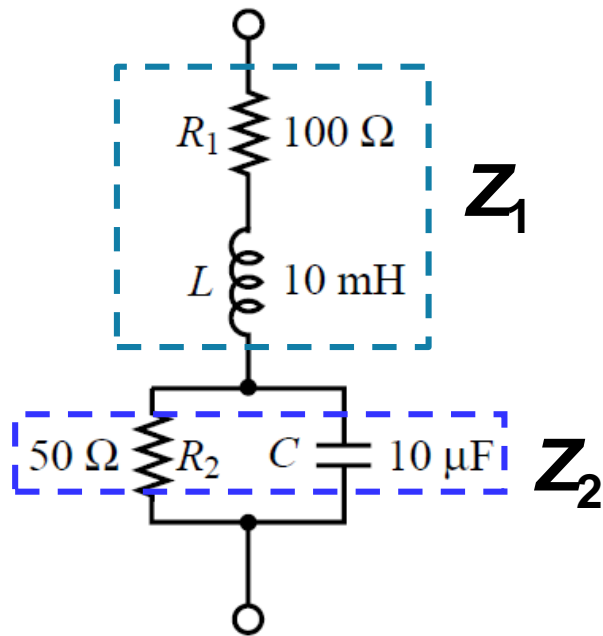

$$Z_1 = Z_{R1} + Z_L = R_1 + j\omega L$$

$$Z_2 = Z_{R2} \parallel Z_C = \frac{Z_{R2}Z_C}{Z_{R2} + Z_C}$$

$$= \frac{R_2 (1/(j\omega C))}{R_2 + 1/(j\omega C)} = \frac{R_2}{1 + j\omega CR_2}$$

Equivalent Impedance

$$Z_{EQ} = Z_1 + Z_2 = R_1 + j\omega L + \frac{R_2}{1 + j\omega CR_2} = 100 + j10^4 \times (10 \times 10^{-3}) + \frac{50}{1 + j10^4 \times (10 \times 10^{-6}) \times 50}$$

$$= 100 + j100 + \frac{50}{1 + j5} = 100 + j100 + 1.92 - j9.62 = 101.92 + j90.38 = 136.2 \angle 0.723^\circ \Omega$$

PROCEDURE FOR AC CIRCUIT ANALYSIS

1. Identify the **sinusoidal source(s)** and note the **excitation frequency**.
2. Convert the **source(s)** to **phasor form**.
3. Represent each **circuit element** by its **impedance**.
4. Solve the resulting **phasor circuit**, using appropriate network analysis tools.
5. Convert the (phasor-form) answer to its **time-domain equivalent**

AC CIRCUIT ANALYSIS WITH *PHASOR AND IMPEDANCE*


Current Node method 电流节点法 and Voltage Mesh (Loop) method 电压网格/回路法 with *Voltage/Current* Phasors

- Kirchhoff's Current Law (KCL)

$$\text{KCL: } \sum_k I_k = 0, \quad \text{for any node}$$

- Kirchhoff's Voltage Law (KVL)
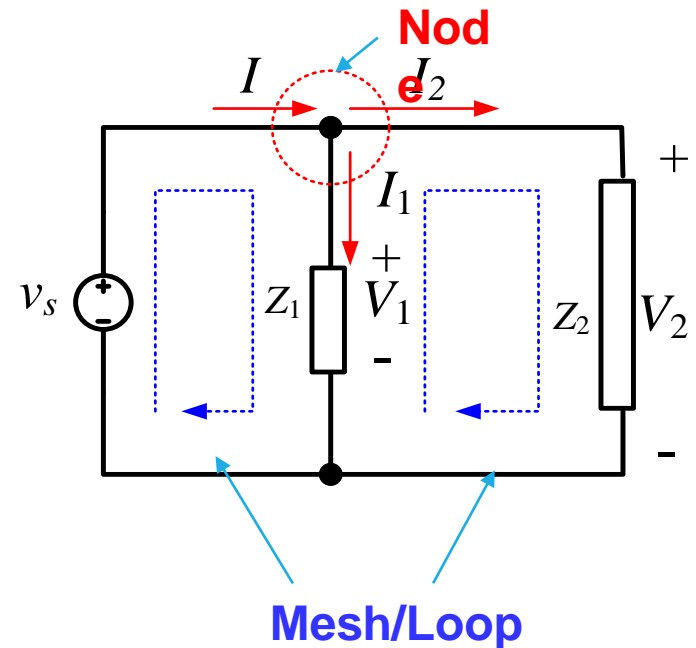
$$\text{KVL: } \sum_k V_k = 0, \quad \text{for any loop}$$



Example – A Simple AC Circuit

Source (Phasor)

$$v_S(t) = 10 \cos(100t) \text{ V}; \omega = 100 \text{ rad/s}$$

$$\mathbf{V}_S(j\omega) = 10 \angle 0 \text{ V.}$$

Circuit Element (Impedance)

$$Z_{R1} = 50 \Omega, Z_{R2} = 200 \Omega, Z_C = 1/(j100 \times 10^{-4}) = -j100 \Omega$$



Voltage Mesh (Loop) method

$$\mathbf{I}_S = \frac{\mathbf{V}_S}{Z_{R1} + Z_{R2} \parallel Z_C} = \frac{\mathbf{V}_S}{R_1 + \frac{R_2}{1 + j\omega C R_2}}$$

$$= 0.083 \angle 0.727 \text{ A}$$

Time Domain

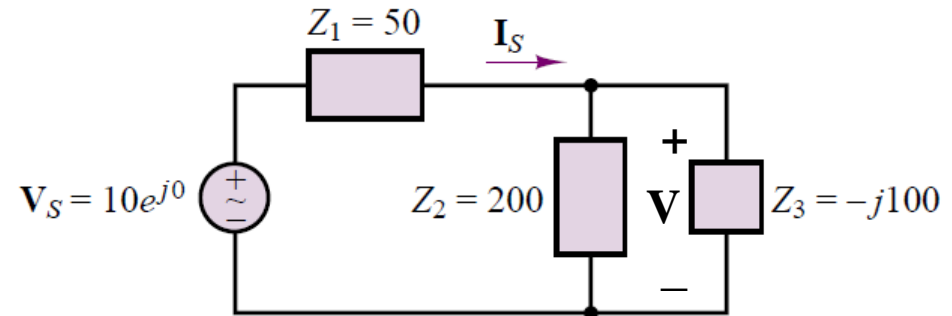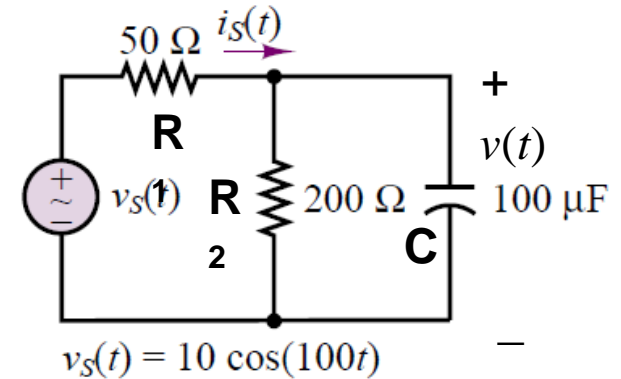
$$i_s(t) = 0.083 \cos(100t + 0.727) \text{ A.}$$



The same circuit in phasor form

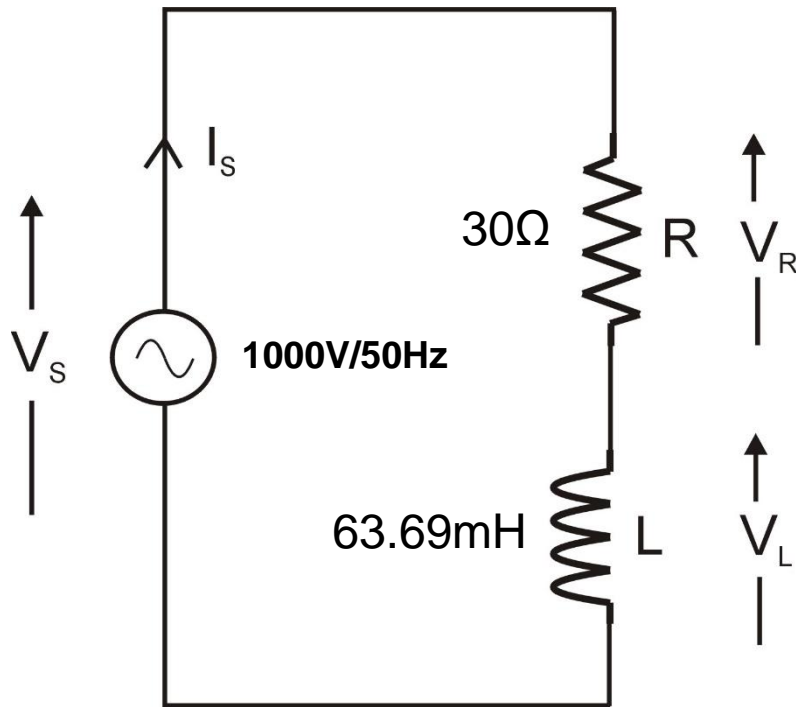Example:

Solution done on whiteboard during lecture



Determine the following:

- 1] The Inductor Reactance X_L
- 2] The Supply Current I_s
- 3] Draw the phasor diagram for the supply voltage and current
- 4] Determine V_R and V_L and add these to the phasor diagram

Note: 1000V is RMS voltage!

TRIGONOMETRY 三角函数

$$(\sin(ax))' = a \cos x, \quad (\cos(ax))' = -a \sin x$$

$$\int \sin(ax) dx = -\frac{1}{a} \cos(ax), \quad \int \cos(ax) dx = \frac{1}{a} \sin(ax)$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos x = \sin\left(x + \frac{\pi}{2}\right) = \sin\left(\frac{\pi}{2} - x\right)$$

$$\sin x = \cos\left(\frac{\pi}{2} - x\right) = -\cos\left(\frac{\pi}{2} + x\right)$$