

## Induction Motors Tutorial

- Q1 Determine the equivalent circuit parameters given the following test results for a 6 pole induction motor:

Locked Rotor Test:

Measurement	Value
$V_{ph}$	100V
$I_s$	5A
$P_{in}$	350W
$R_s$	$6\Omega$

No Load Test:

Measurement	Value
$V_{ph}$	400V
$I_s$	1A
$P_{in}$	100W

Note:  $P_{in}$  is single phase power input (W)

- Q2 A 6 pole, 3 phase, 50Hz induction motor is operating at a speed of 970rpm. The input power is 8kW and the stator copper loss is 240W. Friction and windage loss can be assumed to be zero and the iron loss is 200W. Determine the following:

- (i) Slip (s)
- (ii) Airgap Power (W)
- (iii) Rotor copper loss (W)
- (iv) Mechanical output power (W)
- (v) Torque (Nm)
- (vi) Efficiency (%)

- Q3 Given the equivalent circuit parameters shown on Table 1, determine the following for a 3 phase 4 pole machine rotating at 1350rpm and operating off a 231V (phase voltage), 50Hz supply:

- (i) Slip (s)
- (ii) Airgap Power (W)
- (iii) Mechanical Power (W)
- (iv) Motor Torque (Nm)
- (v) Total Machine Losses (W)
- (vi) Motor Efficiency (%)
- (vii) Input Power (W)
- (viii) Input Current ( $I_s$ ) and power factor

Table 1:

Parameter	Value
$X_M$	$400\Omega$
$R_c$	$1500\Omega$
$R_s$	$5\Omega$
$X_{eq}$	$4\Omega$
$R_r$	$6\Omega$

- Q4 A 7.5kW, 3 phase, 60Hz, 460V, star connected 4 pole machine has a full-load speed of 1764rpm. In the per-phase equivalent circuit; the Stator Resistance is  $0.25\Omega$ , the referred Rotor Resistance is  $0.5\Omega$ , the total Leakage Reactance is  $2.5\Omega$ , and the Magnetising Reactance is  $60\Omega$ . Calculate the ratio between the standstill input current and the full-load input current. What is the full-load power factor? Ignore Iron losses.