

## Transformers

1. A resistive load of  $1.6\Omega$  is connected across the secondary terminals of a  $10\text{kV}/400\text{V}$  transformer. If  $R_c = 50\text{k}\Omega$ ,  $X_m = 10\text{k}\Omega$ ,  $R_{1eq} = 50\Omega$  and  $X_{1eq} = 80\Omega$  calculate:
  - i) The turns ratio
  - ii) The output current ( $I_s$ )
  - iii) The output voltage under load ( $V_s$ )
  - iv) The iron and copper loss
  - v) The magnetising current ( $I_m$ )
  - vi) The Input Current ( $I_p$ )
  - vii) The phasor diagram (include  $V_p$ ,  $V_1$ ,  $V_{R1eq}$ ,  $V_{X1eq}$ ,  $I_p$ ,  $I_1$ ,  $I_m$ ) – drawn to scale
2. Determine the % Voltage Regulation and Efficiency of the transformer in question 1.
3. Determine the necessary secondary load resistance such that the transformer in question 1 operates at its maximum efficiency point.
4. Open-circuit and short-circuit tests were conducted on a  $230/110\text{V}$   $5\text{KVA}$  single-phase transformer and the following results were obtained:

Open-circuit Test:

$$V_1 = 230\text{V} \quad V_2 = 110\text{V} \quad I_1 = 2\text{A} \quad P_{in} = 30\text{W}$$

Short-circuit Test:

$$V_1 = 40\text{V} \quad I_1 = 22\text{A} \quad P_{in} = 200\text{W}$$

Calculate the parameters for the approximate equivalent circuit.

5. For the single phase transformer shown on Figure 1 estimate the maximum input voltage and current at a  $50\text{Hz}$  supply frequency given a maximum flux density ( $B$ ) of  $1.3\text{T}$  and a maximum current density ( $J$ ) of  $2\text{A}/\text{mm}^2$ .

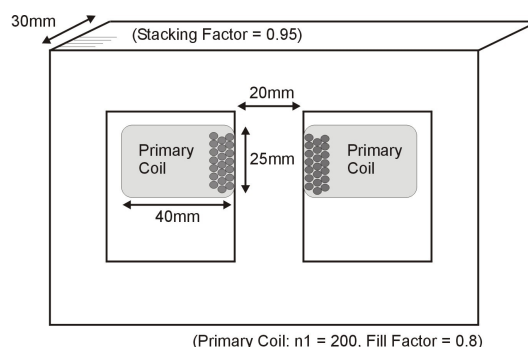


Figure 1

6. A three phase  $12\text{KV}/6.6\text{KV}$  transformer is connected in a  $Y\Delta$ . Determine the phase shift between the input and output line voltages and estimate the Bank Ratio and Phase Ratio for the transformer.