

## Lab 2 Single Phase Transformer Laboratory

### Introduction

Transformers are one of the principle reasons why we have AC Power Networks as opposed to DC systems. Their ability to provide a (relatively!) cheap and reliable means of converting AC voltage levels results in high efficiency AC power transmission. In this series of experiments you will investigate the main features of a small single phase transformer, and by the end of the laboratory you should have a good understanding of the following:

- The Ideal Transformer equations
- The equivalent circuit for a practical single phase transformer
- The Open Circuit & Short Circuit Tests to determine equivalent circuit parameters
- Using the equivalent circuit to predict transformer performance
- Transformer Voltage Regulation & Efficiency under load
- The Transformer Voltage and Current Limits

### Note:

- Before switching on the power supply, ask the demonstrator to check and ensure your circuit connection is correct !!!
- After each experiment measurement, remember to reset the output of the power supply to 0V and turn off the power supply !!!

### Assessment

The 3 laboratory sessions account for 15% of your final mark in Power Engineering 3. You should have with you a bound laboratory book (with graph paper). Record ALL your measured results and any subsequent calculations in your bound laboratory book during the laboratory session, also fill out the necessary results in this lab sheet (this makes it easy for me to check your results during the session).

At some point after the lab session you need to write up the results (neatly!) and complete the associated analysis/theory sections before handing in your lab books before the end of the semester.

Note that you will not be assessed during the laboratory session so please communicate freely with supervisor/demonstrators – we are here to help you obtain accurate results and to help with any questions you have relating to the associated theory.

## Experiment 1: Determining the Transformer Turns Ratio

The equivalent circuit for an **Ideal** Transformer is shown on figure 1 where  $N_P$  is the number of turns on the primary winding and  $N_S$  is the number of turns on the secondary. The corresponding relationships between primary and secondary voltages and currents are as follows:

$$\frac{V_P}{V_S} = \frac{N_P}{N_S} \qquad \frac{I_P}{I_S} = \frac{N_S}{N_P}$$

$N_P/N_S$  is termed the Turns Ratio

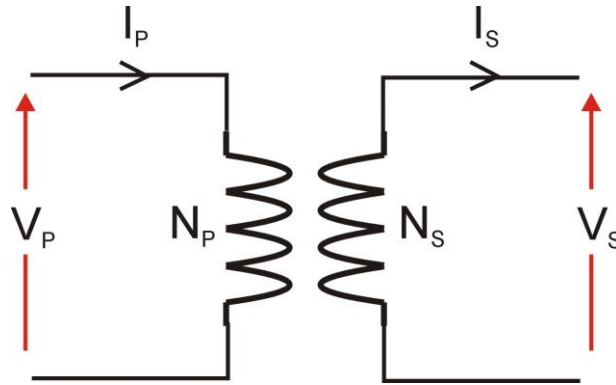


Figure 1: The Ideal Transformer


Clearly the Turns Ratio is very important in defining the operation of a transformer (note: it is used in the equivalent circuit for the practical transformer as well!) and in this first experiment we will determine this turns ratio from measurement:

The experimental setup for this experiment is shown on figure 2. The Turns Ratio can be calculated by measuring the Open Circuit Secondary Voltage ( $V_{SOC}$ ) at a given Primary Voltage ( $V_P$ ) and then using the voltage ratio ( $V_P/V_{SOC}$ ) to calculate the turns ratio.

### Experimental Procedure:

1. Set the AC power supply voltage to zero (**Voltage Adjust** knob should be turned fully counter-clockwise until it hits the end-stop).
2. Select one single-phase transformer on Module DJ11, whose nominal parameters are  $P_N=77V \cdot A$  ,  $U_{1N}/U_{2N}=220/55V$  ,  $I_{1N}/I_{2N}=0.35/1.4A$ . Connect the power supply, meters and transformer as shown in Figure 2, where secondary side of the transformer is open circuit.
3. Turn on the AC power supply.
4. Adjust AC power supply voltage (using Voltage Adjust knob) until approximately the primary side voltage  $V_P=1.2U_{2N}$  (**about 66V**) at the

- primary side of the transformer is displayed on the Voltmeter. Record the primary side voltage  $V_P$  and secondary side voltage  $V_{Soc}$  in the Table 1.
5. Gradually reduce the primary side voltage  $V_P$ . Record  $V_P$  and  $V_{Soc}$  within the range of  $V_P = 1.2 \sim 0.3 U_{2N}$ .
  6. Adjust the AC power supply voltage to zero.
  7. Turn off the AC power supply.

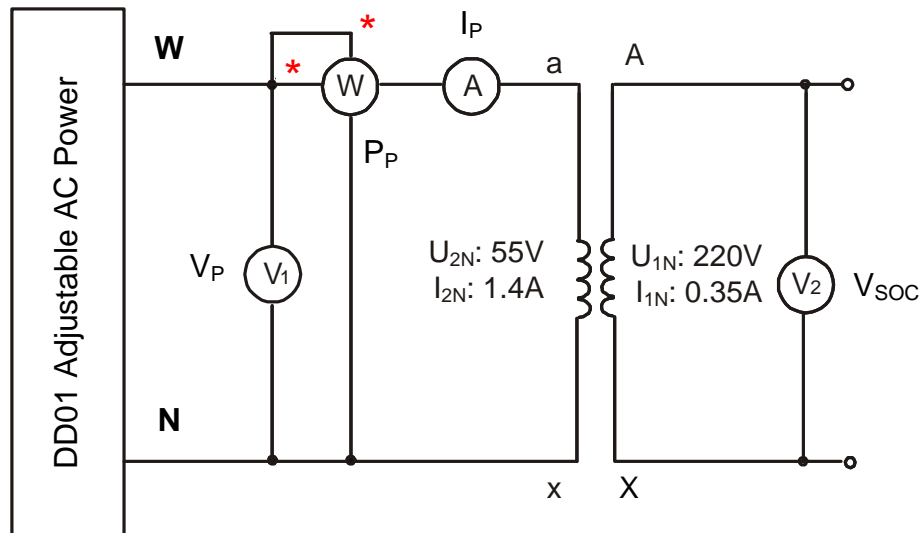

**Figure 2: Experiment 1 Setup**

Using the measured values of primary and secondary voltages, and the Ideal Transformer voltage equation shown above determine the transformer Turns Ratio:

**Table 1. Turns Ratio Test**

No.	1	2	3	4	5
$V_P$ (V)					
$V_{soc}$ (V)					
<b>Turns Ratio</b>					
No.	6	7	8	9	10
$V_P$ (V)					
$V_{soc}$ (V)					
<b>Turns Ratio</b>					

**Note:** The low voltage side winding (i.e. primary side nominal values are 55V 1.4A) of the transformer is connected to the power supply, the high voltage side winding acts as the secondary side.

## Experiment 2: Determining the practical Transformer Equivalent Circuit

As will be outlined in the lectures the practical transformer has an equivalent circuit which takes into account issues such as wiring copper loss, leakage inductance, magnetising current and iron loss. The complete equivalent circuit for a transformer is shown on Figure 3.

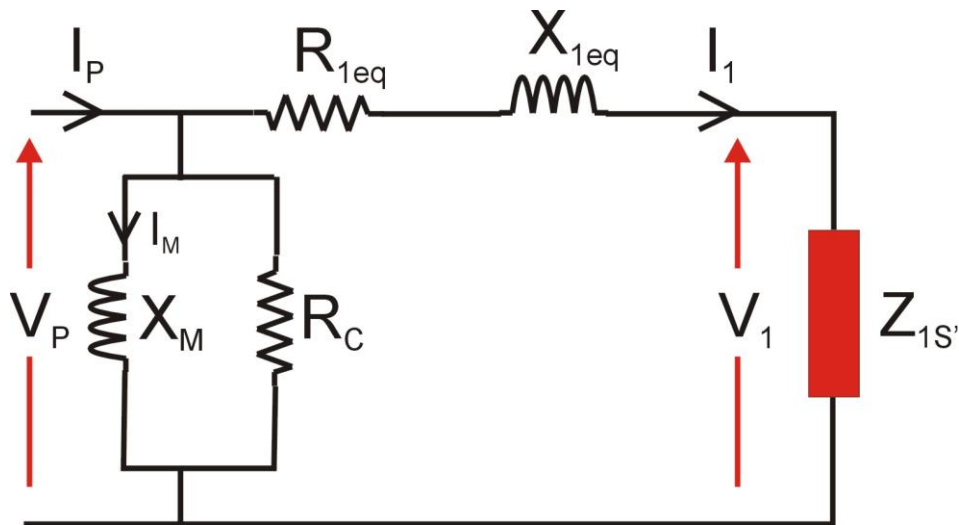


Figure 3: Transformer Equivalent Circuit

The purpose of the next couple of tests is to determine values for the transformer parameters  $R_{1eq}$ ,  $X_{1eq}$ ,  $X_M$  and  $R_C$ .

### Experiment 2A: Open Circuit Test (to determine $X_M$ and $R_C$ )

In this experiment the secondary winding is open circuit ( $Z_{1S'}$  is Open Circuit) and therefore  $I_1 = 0A$  and the equivalent circuit simplifies to that shown on Figure 4.

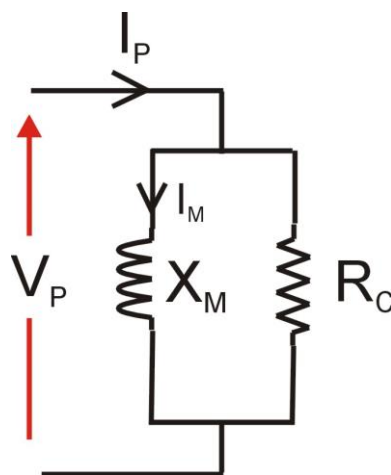


Figure 4: Open Circuit Test Equivalent Circuit

Notice that we have one resistive component  $R_C$  and one inductive component  $X_M$ . By knowing (hopefully!) that **REAL** Power is associated with the resistance and **REACTIVE** power is associated with inductance we can determine each of these components by simply measuring

primary voltage ( $V_P$ ), primary current ( $I_P$ ) and primary real power ( $W$ ) and using the following primary circuit relationships:

Parameter	Units	Equation
Real Power	W	$P_P = \frac{V_P^2}{R_C}$
Apparent Power	VA	$S_P = V_P \cdot I_P$
Reactive Power	VAr	$Q_P = \sqrt{(S_P^2 - P_P^2)}$
Reactive Power	VAr	$Q_P = \frac{V_P^2}{X_M}$

For the circuit shown in Figure 2, repeat the test outlined in Experiment 1 but this time record primary voltage ( $V_P$ ), primary current ( $I_P$ ) and primary real power ( $P_P$ ). From test results and above equations determine values for  $R_C$  and  $X_M$ :


Table 2. Open Circuit Test

No.	1	2	3	4	5
$V_P$ (V)					
$I_P$ (A)					
$P_P$ (W)					
$S_P$ (VA)					
$Q_P$ (VAr)					
$X_M$ ( $\Omega$ )					
$R_C$ ( $\Omega$ )					
No.	6	7	8	9	10
$V_P$ (V)					
$I_P$ (A)					
$P_P$ (W)					
$S_P$ (VA)					
$Q_P$ (VAr)					
$X_M$ ( $\Omega$ )					
$R_C$ ( $\Omega$ )					

**Note:** The Power Meter current and power values may be in milliamps and milliwatts

## Experiment 2B: Short Circuit Test (to determine $R_{1eq}$ and $X_{1eq}$ )

In this experiment (see next page for setup) the secondary winding is short circuit ( $Z_{1s} = 0\Omega$ ) and as a result  $I_1$  current will flow in the primary. Under short circuit conditions  $I_1$  is very much bigger than magnetising and iron loss currents and so these elements can be ignored and the equivalent circuit simplifies to that shown on figure 5.

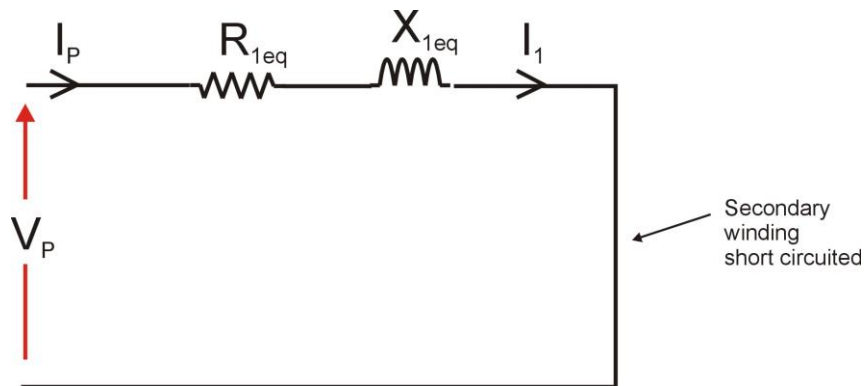


**Figure 5: Short Circuit Test Equivalent Circuit**

Once again we have one resistive component ( $R_{1eq}$ ) and one inductive component ( $X_{1eq}$ ) so knowing that **REAL** Power is associated with the resistance and **REACTIVE** power is associated with inductance we can determine each of these components by simply measuring primary voltage ( $V_P$ ), primary current ( $I_P$ ) and primary real power ( $P_P$ ) and using the following relationships:

Parameter	Units	Equation
Real Power	W	$P_P = I_P^2 \cdot R_{1eq}$
Apparent Power	VA	$S_P = V_P \cdot I_P$
Reactive Power	VAr	$Q_P = \sqrt{(S_P^2 - P_P^2)}$
Reactive Power	VAr	$Q_P = I_P^2 \cdot X_{1eq}$

The experimental setup is shown on Figure 6.

**Note** that this test is carried out at **reduced** supply voltage so ensure the AC power supply voltage is set to **zero** before switching on !!!

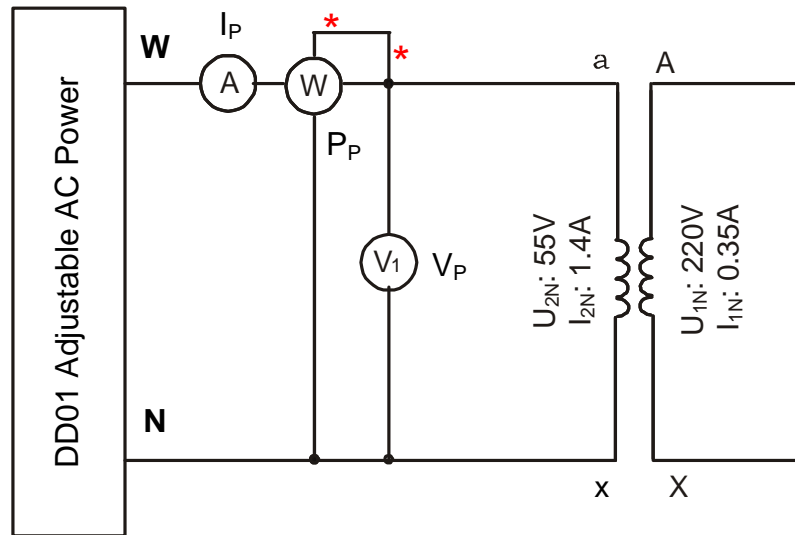

**Figure 6: Short Circuit Test Setup**

### Experimental Procedure:

1. Turn off the AC power supply and set the AC voltage to zero.
2. Connect a short circuit wire across the transformer Secondary winding as shown on Figure 6, where secondary side of the transformer is short circuit.
3. Turn on the AC power supply and **slowly** increase the voltage until approximately the primary current  $I_P = 1.1 I_{2N} \approx 1.54A$ . ( **$V_P$  is about 7 volts !!!**)
4. Gradually reduce the primary voltage  $V_P$ , record voltage ( $V_P$ ), current ( $I_P$ ) and power ( $P_P$ ) within the range of  $I_P = 0.2 \sim 1.1 I_{2N}$ .
5. Reduce the AC voltage to zero and turn off the AC power supply.
6. From the test results and above equations determine values for  $R_{1eq}$  and  $X_{1eq}$ .

**Note:** If Primary Real Power > Primary Apparent Power then assume  $Q_P = 0$  (this is a result of some assumptions in the equivalent circuit which are not valid for a transformer this size)

**If you found any meter reading is weird (too larger or smaller than expected value), please turn off the power supply and set the AC voltage to zero immediately!!! Recheck your circuit connection!!!**


Table 3. Short Circuit Test

No.	1	2	3	4	5
$V_P$ (V)					
$I_P$ (A)					
$P_P$ (W)					
$S_P$ (VA)					
$Q_P$ (VAr)					
$X_{1eq}$ ( $\Omega$ )					
$R_{1eq}$ ( $\Omega$ )					
No.	6	7	8	9	10
$V_P$ (V)					
$I_P$ (A)					
$P_P$ (W)					
$S_P$ (VA)					
$Q_P$ (VAr)					
$X_{1eq}$ ( $\Omega$ )					
$R_{1eq}$ ( $\Omega$ )					

**Note:** The low voltage side winding (i.e. primary side nominal values are 55V 1.4A) of the transformer is connected to the power supply, the high voltage side winding acts as the secondary side.



From your results fill in the component values of the complete transformer equivalent circuit shown on Figure 7. Also note that the value of  $Z_{1s'}$  (secondary load impedance REFERRED TO THE PRIMARY SIDE) is equal to the  $(\text{turns ratio})^2 \times \text{Secondary Impedance } (Z_s)$ . Calculate the value for  $(\text{turns ratio})^2$  based on your measured value for turns ratio and put this value in the box below  $Z_{1s'}$  in Figure 7.

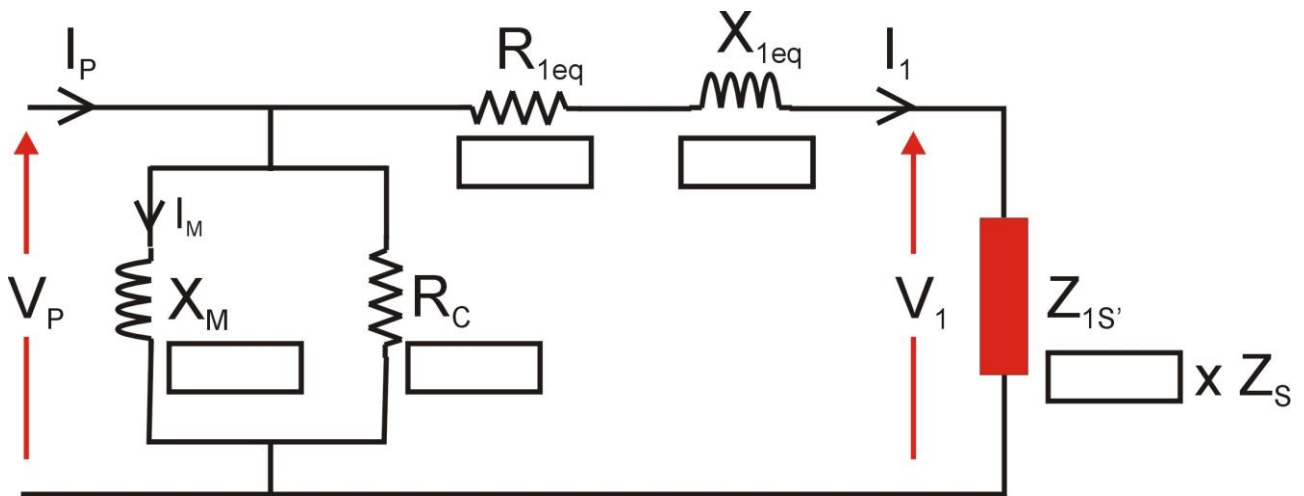

**Figure 7: Measured Transformer Equivalent Circuit**

### Using the Equivalent Circuit to Predict Transformer Performance

The purpose of the equivalent circuit is to be able to predict transformer performance (output voltage, current, power, efficiency etc) for a given load. You can therefore use your equivalent circuit to calculate transformer performance for a given secondary load impedance and input voltage.

#### Theory:

Calculate the following parameters using your equivalent circuit for a primary voltage ( $V_P$ ) of 55V and a  $628\Omega$  load resistance ( $Z_s$ ) connected across the secondary winding:

1. Output Current ( $I_s$ )
2. Output Voltage ( $V_s$ ) - plot this value on the previous graph of Output Voltage v Output Current
3. Output Power
4. Voltage Regulation
5. Transformer Copper Loss (W) (hint: associated with  $R_{1eq}$ )
6. Transformer Iron Loss (W) (hint: associated with  $R_c$ )
7. Transformer Efficiency

**Note: The low voltage side winding (i.e. primary side nominal values are 55V 1.4A) of the transformer is connected to the power supply, the high voltage side winding (i.e. secondary side nominal value is 220 0.35A) is connected to the load resistance.**

**Steps:**

1. Calculate  $Z_{1s'}$  based on  $(\text{turns ratio})^2 \times 628\Omega$
2. Using the equivalent circuit on Figure 7 calculate  $I_1$  (hint: ignore  $X_m$  and  $R_c$  components)
3. Using the equivalent circuit on Figure 7 calculate  $V_1$  (hint:  $V_1 = I_1 \cdot Z_{1s'}$ )
4. The secondary output voltage and current are derived from  $I_1$  and  $V_1$  through the following relationships (where  $N_p/N_s$  is the turns ratio):

$$V_s = \frac{N_s}{N_p} \cdot V_1 \quad I_s = \frac{N_p}{N_s} \cdot I_1$$

Parameter	Value	Units
Output Current ( $I_s$ )		
Output Voltage ( $V_s$ )		
Output Power		
Voltage Regulation <sup>*1</sup>		
Transformer Copper Loss		
Transformer Iron Loss		
Transformer Efficiency <sup>*1</sup>		

<sup>\*1</sup> See next page for definitions of Voltage Regulation & Efficiency

### Experiment 3: Transformer Regulation & Efficiency

We'll leave the equivalent circuit for the time being and now look at transformer operation with an actual load connected to the secondary winding. Invariably we want the load to dissipate real power so we will represent this with a simple value of resistance. When we investigate transformer performance we are primarily interested in the following:

- Transformer Voltage Regulation
- Transformer Efficiency

Voltage Regulation is a measure of how well the output voltage ( $V_s$ ) remains constant from no load (open circuit) to full load (maximum  $I_s$ ). It is expressed mathematically as:

$$\text{Voltage Regulation} = \frac{V_{\text{SOC}} - V_{\text{SL}}}{V_{\text{SOC}}} \times 100\%$$

where:

$V_{\text{SOC}}$  = Open Circuit Secondary Voltage  
 $V_{\text{SL}}$  = Secondary Voltage under load

Given that we want the output voltage to remain as close as possible to the open circuit voltage we therefore want the Regulation value to be as low as possible (typically <5%).

Transformer Efficiency is expressed mathematically using any one of the following equations:


$$\text{Efficiency} = \frac{\text{Output Power (W)}}{\text{Input Power (W)}} \times 100\%$$

$$\text{Efficiency} = \frac{\text{Output Power (W)}}{\text{Output Power (W)} + \text{Losses (W)}} \times 100\%$$

$$\text{Efficiency} = \frac{\text{Input Power (W)} - \text{Losses (W)}}{\text{Input Power}} \times 100\%$$

The aims of the following series of tests is to measure performance at four different resistive load points, and from the results calculate the Voltage Regulation and Efficiency at each point. The experimental set up is shown on Figure 8. The general idea is to measure input and output voltages, currents and powers over the load range for a constant input voltage ( $V_P$ ).

Note: **The low voltage side winding (i.e. primary side nominal values are 55V 1.4A) of the transformer is connected to the power supply, the high voltage side winding (i.e. secondary side nominal value is 220 0.35A) is connected to the load resistance  $R_L$  via Switch  $S_1$ .**  $R_L$  is the series four 900  $\Omega$  (max current 0.41A) variable resistors in Module D42, Switch  $S_1$  is the switch  $S_1$  in Module D51.

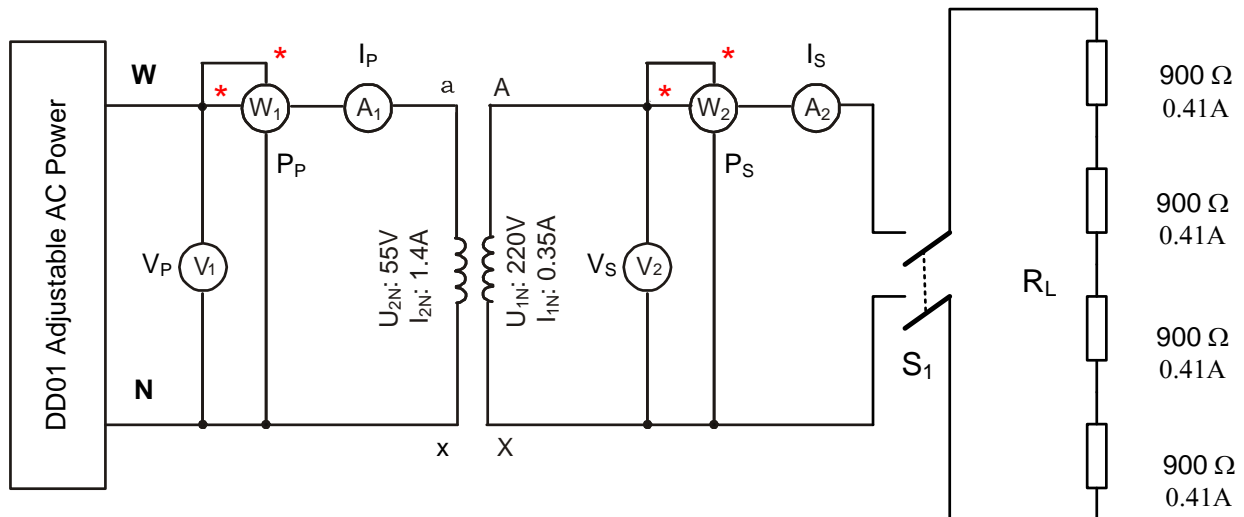

**Figure 8: Transformer Regulation & Efficiency Tests**

### **Experimental Procedure:**

1. Turn off the AC power supply and set the AC voltage to zero.
2. Connect the resistors to the Secondary winding as shown on Figure 8. Adjust the value of the series four resistor  $R_L$  to its maximum value (about  $3600\Omega$ )
3. Turn on the AC power supply and adjust until approximately 55V. Gradually reduce the resistor the value of resistor  $R_L$  until the secondary current  $I_s = I_{1N}/4$ ,  $I_{1N}/2$ ,  $3 \cdot I_{1N}/4$ , and  $I_{1N}$ , measure primary circuit parameters: voltage ( $V_P$ ), current ( $I_P$ ) and real power ( $P_P$ ) and secondary circuit parameters: voltage ( $V_s$ ), current ( $I_s$ ) and real power ( $P_s$ ), respectively.
4. Repeat for Open Circuit Secondary condition (no resistors connected) but only measure the Secondary voltage ( $V_{soc}$ ).
5. Turn off the AC power supply.

From your test results and associated equations calculate the Voltage Regulation and transformer Efficiency at each of the four load points:

$V_{SOC}$	
-----------	--

Load Point	$V_P$	$I_P$	$P_P$		$V_S$	$I_S$	$P_S$		Regulation	Efficiency
	(V)	(A)	(W)		(V)	(A)	(W)		(%)	(%)
$R_L=900$										
$R_L=1800$										
$R_L=2700$										
$R_L=3600$										
Open Circuit										

From the results plot Secondary Voltage ( $V_S$ ) and Efficiency against Output Current  $I_S$  (note using a false zero on the Y axis values is recommended to maximise resolution):

### Analysis of Results and Comparison with Theory

Using your results for  $I_S=I_{1N}$  (i.e.  $628\Omega$  load) complete the following table of comparison between your measured results and your theoretical values calculated earlier from your equivalent circuit:

Parameter	Measured	Theory	Units
Output Current ( $I_S$ )			
Output Voltage ( $V_S$ )			
Output Power			
Voltage Regulation			
Transformer Efficiency			